

IIND YEAR
EES451
LINEAR INTEGRATED CIRCUITS
AND
APPLICATIONS
UNIT-III
APPLICATIONS OF OP-AMP

INSTRUMENTATION AMPLIFIER:

* In a number of industrial and consumer applications, one is required to measure and control physical quantities.

* Some typical examples are measurement and control of temperature, humidity, light intensity.

* These quantities are measured with the help of transducers.

* The output of transducer has to be amplified so that it can drive the indicator or display system.

FEATURES OF INSTRUMENTATION AMPLIFIER:

- * high gain accuracy
- * high CMRR
- * high gain stability with low temperature coefficient
- * low dc offset
- * low output impedance.

$$V_o = -\frac{R_2}{R_1} V_2 + \frac{1}{1 + \frac{R_3}{R_4}} V_1 \left(1 + \frac{R_2}{R_1} \right)$$

$$V_o = \frac{-R_2}{R_1} \left[V_2 - \frac{1}{1 + \frac{R_3}{R_4}} \left(\frac{R_1 + 1}{R_1} \right) V_1 \right]$$

$$\text{For } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$V_o = \frac{R_2}{R_1} (V_1 - V_2)$$

* The op-amps A_1 and A_2 have differential input voltage as zero.

* For $V_1 = V_2$, that is under common mode operation the voltage across R will be zero.

* As no current flows through R and R' the non-inverting amplifier A_1 acts as voltage follower.

* So its output $V_2' = V_2$.


* Similarly op-amp A_2 acts as voltage follower having output $V_1' = V_1$.

* If $V_1 \neq V_2$, current flows in R and R' and $(V_2' - V_1') > (V_2 - V_1)$

* Therefore this circuit has differential gain and CMRR more compared.

$$V_o = -\frac{R_2}{R_1} V_2' + \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2 V_1'}{R_1 + R_2}\right)$$

$$= \frac{R_2}{R_1} (V_1' - V_2')$$

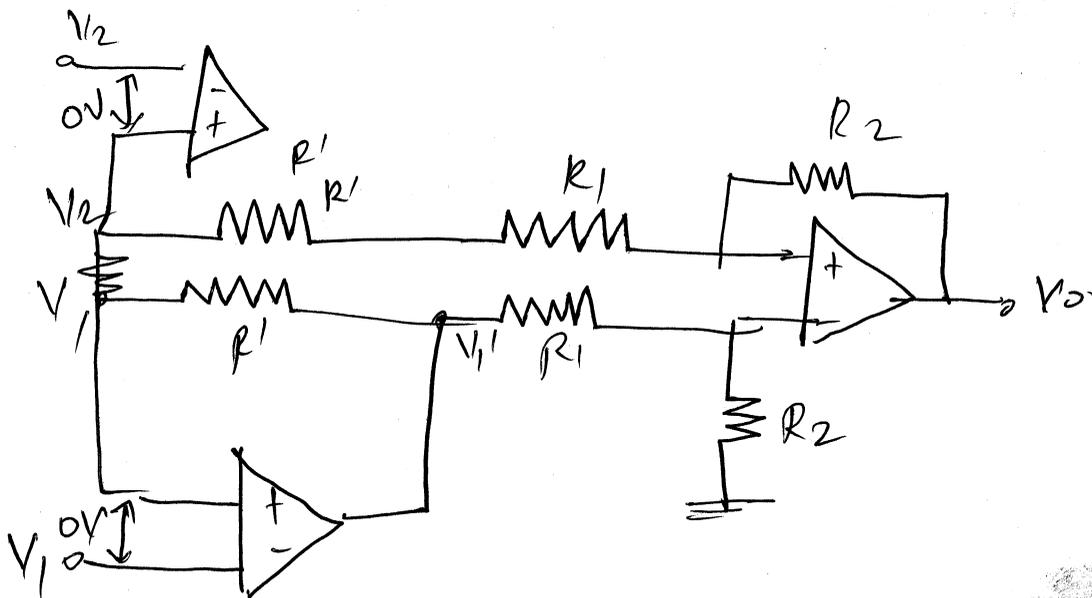

SQUARE WAVE GENERATORS:

* Besides generating sine waves, the op-amp generates square wave form and pulses, an active device generate a square waveform is also called as multivibrator.


(i) Astable multivibrator

* It is also called as free running oscillator, the principle of generation of square wave output is to force an op-amp to operate in the saturation region.

$$\beta = \frac{R_2}{R_1 + R_2}$$

* The output is also fed back to inverting terminal input after integrating by low pass RC combination.

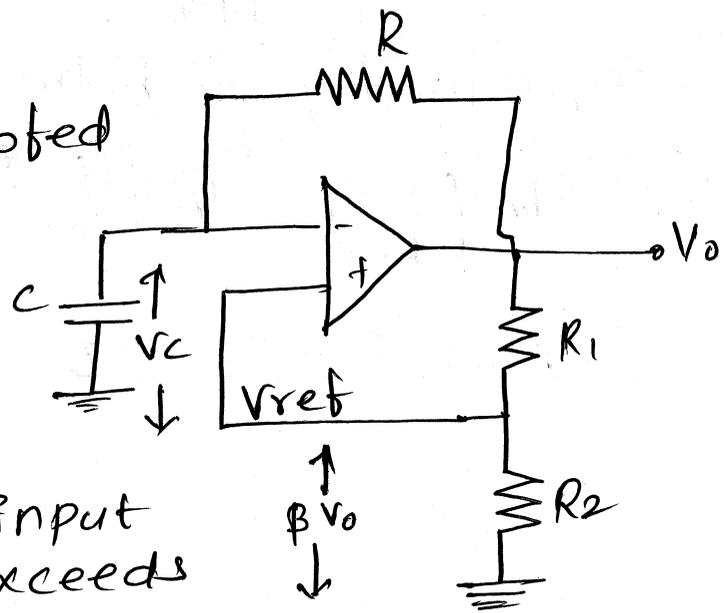* Whenever the input at (-) input just exceeds V_{ref} switching takes place to $+V_{sat}$ to $-V_{sat}$.



$$V_c(t) = V_f + (V_i - V_f) e^{-t/RC}$$

$$\begin{aligned} V_f &= +V_{sat} \\ V_i &= -\beta V_{sat} \end{aligned}$$

considering

$$V_c(t) = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-t/RC}$$

at $t = T_1$

$$V_c(t) = \beta V_{sat}$$

$$\beta V_{sat} = V_{sat} - (\beta V_{sat} + V_{sat}) e^{-T_1/RC}$$

$$\beta V_{sat} - V_{sat} = -V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$V_{sat} (\beta - 1) = -V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$V_{sat} (1 - \beta) = V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$e^{-T_1/RC} = \frac{1 - \beta}{1 + \beta}$$

Taking log on both sides

$$\ln\left(\frac{-T_1}{RC}\right) = \ln\left(\frac{1 - \beta}{1 + \beta}\right)$$

considering $\beta = 0.5$


$$\frac{-T_1}{RC} = \ln\left(\frac{1 - 0.5}{1 + 0.5}\right)$$

$$\frac{-T_1}{RC} = \ln\left(\frac{0.5}{1.5}\right)$$

$$\frac{-T_1}{RC} = \ln\left(\frac{1}{3}\right)$$

$$\boxed{T_1 = 1.1 RC}$$

(ii) MONOSTABLE MULTIVIBRATOR!

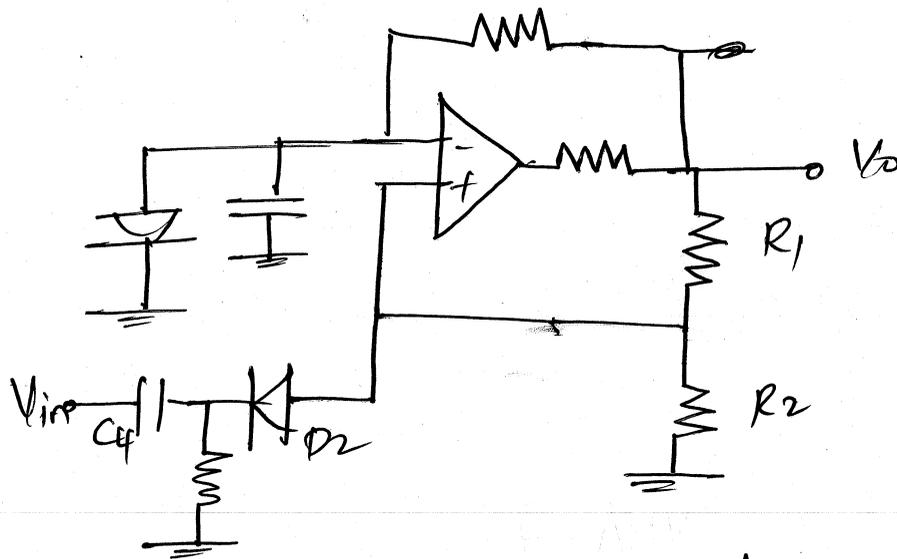

* It has one stable state and one quasi stable state.

* This circuit is useful for generating single output pulse of adjustable time duration in response to a triggering signal.

* The width of output signal depends only on external components connected to the op-amp.

* Diode D_1 clamps the capacitor voltage to $0.7V$ when output is $+V_{sat}$.

* A negative going pulse signal of magnitude V_i passing through differentiator $R_4 C_2$ and diode D_2 produces going triggering impulse and is applied to the (+) input terminal.

$$V_o = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_f = -V_{sat}$$

$$V_i = V_D$$

$$V_o = -V_{sat} + (V_D + V_{sat}) e^{-t/RC}$$

$$\text{At } t = T, V_o = -\beta V_{sat}$$

$$- \beta V_{sat} = -V_{sat} + (V_D + V_{sat}) e^{-T/RC}$$

$$- \beta V_{sat} + V_{sat} = (V_D + V_{sat}) e^{-T/RC}$$

$$\frac{V_{sat}(1-\beta)}{V_D + V_{sat}} = e^{-T/RC}$$

$$\frac{V_{sat}(1-\beta)}{V_{sat}(1 + \frac{V_D}{V_{sat}})} = e^{-T/RC}$$

$$\frac{-T}{RC} = \ln \left(\frac{1 + \frac{V_D}{V_{sat}}}{1-\beta} \right)$$

$$T = RC \ln \left(\frac{1 + \frac{V_D}{V_{sat}}}{1-\beta} \right)$$

$$V_{sat} \gg V_D$$

$$R_1 = R_2$$

$$\beta = 0.5$$


$$\boxed{T = 0.69 RC}$$

* Monostable multivibrator circuits are also referred to as time delay circuits as they generate a fast transition at a predetermined time T after the application of an input trigger.

TRIANGULAR WAVE GENERATOR:

* Generally triangular wave generator may be derived from other sources through the use of comparators.

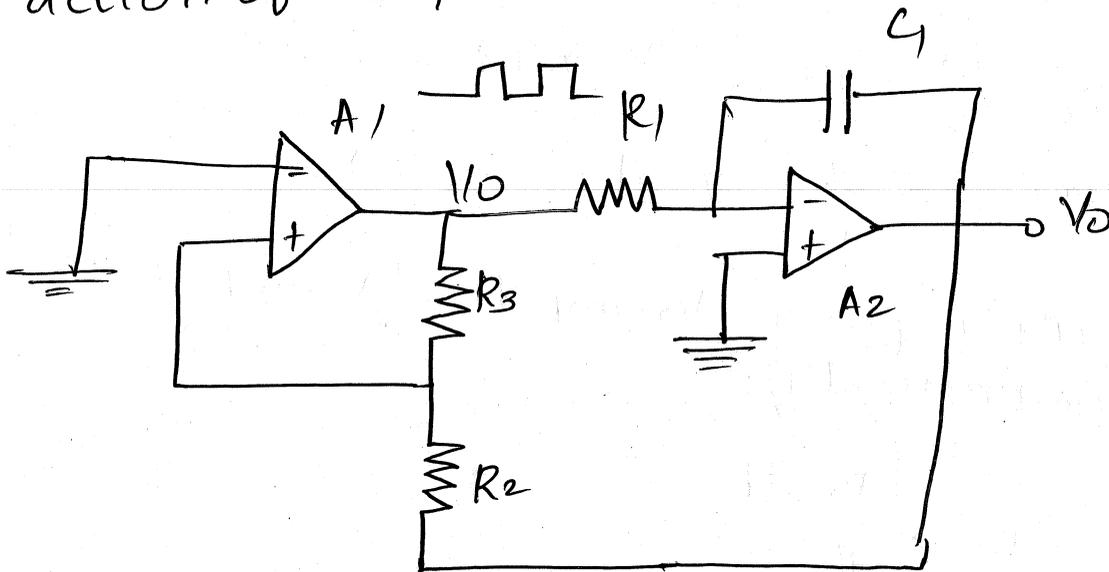* Linear wave forms such as triangle and ramps may be derived from the charge/discharge action of a capacitor.



* It basically consists of two level comparator followed by integrator circuit. The output of A_1 is a square wave of amplitude $\pm V_{sat}$ and is applied to the (-) i/p of the integrator producing a triangular wave.

$$P = V_f + (V_i - V_f) \beta$$

$$V_f = -V_{ramp}$$

$$V_i = +V_{sat}$$

$$\beta = \frac{R_2}{R_2 + R_3}$$

$$P = -V_{ramp} + (V_{sat} + V_{ramp}) \frac{R_2}{R_2 + R_3}$$

At; $t = t_1$; Voltage at p becomes equal to zero

$$-V_{\text{ramp}} = -\frac{R_2}{R_3} (+V_{\text{sat}}) \quad \text{--- (1)}$$

at $t = t_2$, when output of A_1 switches from $-V_{\text{sat}}$ to $+V_{\text{sat}}$

$$V_{\text{ramp}} = -\frac{R_2}{R_3} (-V_{\text{sat}}) \quad \text{--- (2)}$$

Peak to peak value of output is

$$V_o(\text{PP}) = +V_{\text{ramp}} - (-V_{\text{ramp}})$$

$$V_o(\text{PP}) = 2 \frac{R_2}{R_3} V_{\text{sat}} \quad \text{--- (3)}$$

The output from $-V_{\text{ramp}}$ to $+V_{\text{ramp}}$ in half the time period $T/2$

$$V_o = -\frac{1}{RC} \int v_i dt$$

$$V_o(\text{PP}) = -\frac{1}{R_1 C_1} \int_0^{T/2} (-V_{\text{sat}}) dt$$

$$= \frac{V_{\text{sat}}}{R_1 C_1} \left(\frac{T}{2} \right)$$

$$T = 2 R_1 C_1 \frac{V_o(\text{PP})}{V_{\text{sat}}} \quad \text{--- (4)}$$

Putting $V_o(\text{PP})$ Value

$$T = 2 R_1 C_1 \frac{2 \frac{R_2}{R_3} V_{\text{sat}}}{V_{\text{sat}}}$$

$$= \frac{4 R_1 C_1 R_2}{R_3}$$

$$\boxed{f_0 = \frac{1}{T} = \frac{R_3}{4 R_1 C_1 R_2}}$$

WRITE IN DETAIL ABOUT ANALOG MULTIPLIER AND ITS APPLICATIONS?

* Transistors and operational amplifiers used to design Analog multiplier ICs.

* A Multiplier produces an output V_o which is proportional to the product of two inputs V_x and V_y .

* Quadrant defines the applicability of the circuit to bipolar signs at the inputs

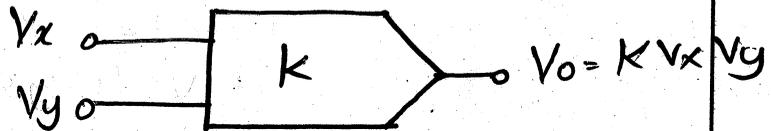


FIG. MULTIPLIER SYMBOL

First Quadrant \rightarrow only positive input signals

Two Quadrants \rightarrow one bipolar and one unipolar signal

Four Quadrants \rightarrow Two Bipolar signal.

Multiplier performance is specified in terms of accuracy and non-linearity.


Accuracy: Represents the maximum deviation of the actual output from the ideal value. This deviation also referred to as total error.

Non-linearity: * Also referred as linearity error. * maximum output deviation from the best straight for the case where one i/p is varied from one end to end and other end is kept fixed.

MULTIPLIER MODES OF OPERATION:

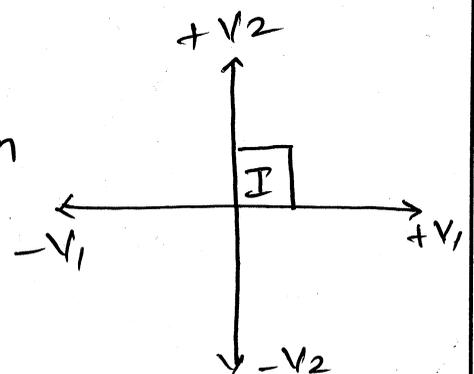
(i) one quadrant multiplier:

* In this modes of operation of a multiplier, both the input signal V_1 and V_2 are positive polarity.



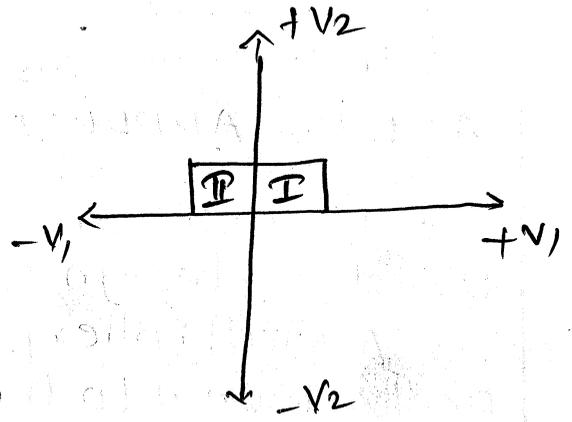
(ii) Two quadrant multiplier:

* In this mode of operation of a multiplier one of the input V_1 or V_2 held positive, and another input allowed to swing both positive and negative.



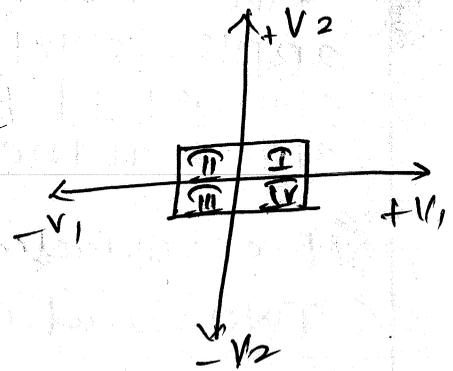(iii) Four quadrant multiplier:

* In this mode of operation both the input voltages V_1 and V_2 swings both positive and negative.



FEATURES:

- * High input impedance
- * Laser trimmed 10V scaling reference
- * No external components required
- * Supply voltage ranging from +8V to +18V

APPLICATIONS:

(i) FREQUENCY DOUBLER

Let $V_1 = V_x \sin \omega t$

$V_2 = V_y \sin \omega t$

Generally multiplier output

$$V_o = \frac{V_1 \cdot V_2}{V_{ref}}$$

$$V_o = \frac{V_x \cdot V_y \sin^2 \omega t}{V_{ref}}$$


$\sin^2 \theta = \frac{1 - \cos 2\theta}{2}$

* The output contains a dc term and negative cosine wave of double frequency.

$$V_o = \frac{V_x \cdot V_y}{V_{ref}} \left(\frac{1 - \cos 2\omega t}{2} \right)$$

The dc term can be easily removed by using 1μF coupling capacitor b/w load and o/p terminal
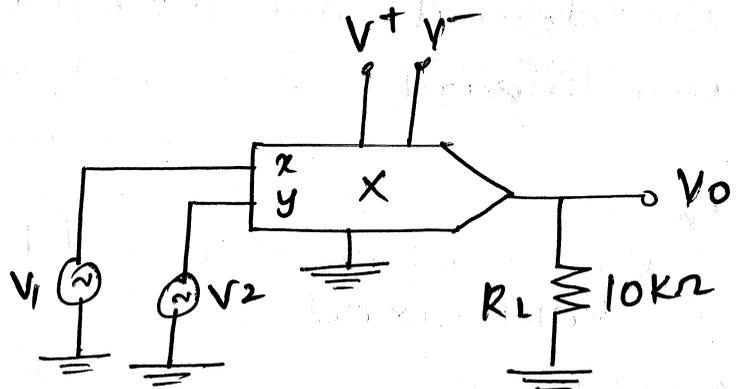
$$V_o = \frac{V_x \cdot V_y}{2 \cdot V_{ref}} - \frac{V_x \cdot V_y \cos 2\omega t}{2 \cdot V_{ref}}$$



(ii) VOLTAGE SQUARER

* Let sine wave voltage $V_i = V_m \sin \omega t$ applied on both the inputs then the output voltage V_o .


$$V_o = \frac{V_i^2}{V_{ref}}$$

$$K = \frac{V_o}{V_i^2} \text{ (or) } V_o = K V_i^2$$

example: V_i^2

$$V_i = 5 \sin 2\pi \times 10^4 t$$

$$V_{ref} = 10V$$

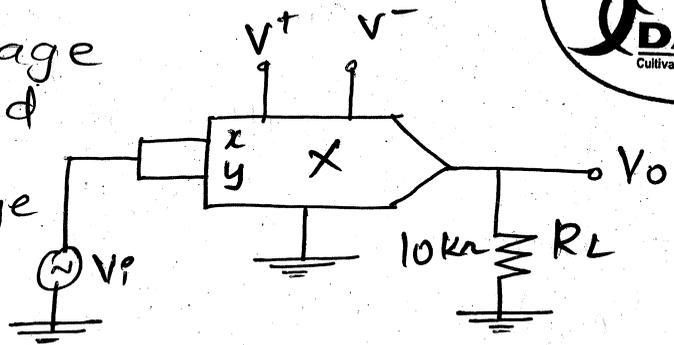


$$V_o = \frac{5^2 (\sin 2\pi \times 10^4 t)^2}{10}$$

$$= 2.5 \left(\frac{1}{2} - \frac{1}{2} \cos 2\pi \times 2 \times 10^4 t \right)$$

$$= 1.25 - 1.25 \cos 2\pi \times 2 \times 10^4 t$$

(iii) VOLTAGE DIVIDER:

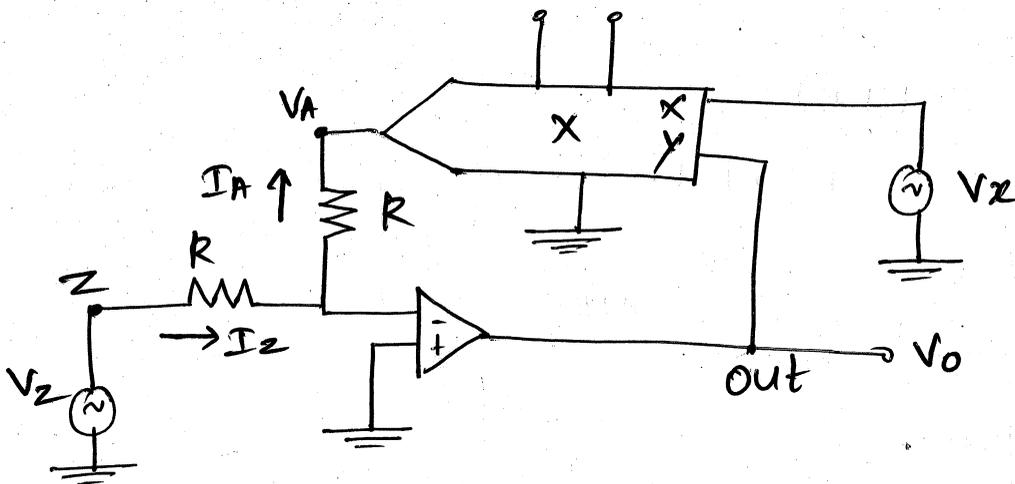

* Division is the complement of multiplication. Can be design by placing the multiplier circuit element in the op-amp feedback loop.

The output voltage V_A of the amplifier.

$$V_A = \frac{V_z V_y}{V_{ref}} = \frac{V_x V_o}{V_{ref}}$$

$$V_A = -I_A R$$

$$I_A = -\frac{V_A}{R}; \quad I_A = -\frac{V_x V_o}{R V_{ref}}$$

$$\therefore I_z = I_A$$


$$I_z = -\frac{V_z V_o}{V_{ref} R}$$

$$V_z = I_z R = -\frac{V_z V_o}{V_{ref}}$$

$$V_o = -V_{ref} \frac{V_z}{V_z}$$

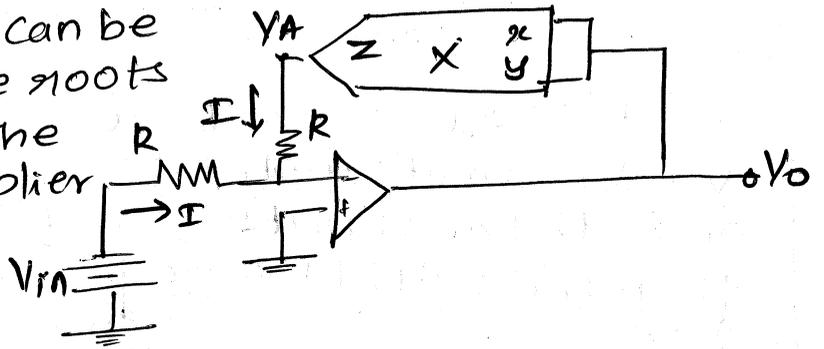(IV) SQUARE ROOTER:

* A divider circuit can be used to find square roots by connecting both the inputs of the multiplier to the output of an OP-amp.



$$V_A = \frac{V_o^2}{V_{ref}}$$

$$V_A = -V_{in}$$

$$-V_{in} = \frac{V_o^2}{V_{ref}}$$

$$V_o^2 = -V_{in} V_{ref}$$

$$V_o = \sqrt{V_{in} V_{ref}}$$

* Thus the output voltage is square rooter by connecting both the inputs of the multiplier.

(V) PHASE ANGLE DETECTION:

$$V_1 = V_x \sin \omega t$$

$$V_2 = V_y \sin(\omega t + \theta)$$


$$V_o = \frac{V_x V_y}{V_{ref}} \sin \omega t \sin(\omega t + \theta)$$

$$\sin A \sin B = \frac{1}{2} [\cos(A-B) - \cos(A+B)]$$

$$= \frac{1}{2} [\cos(\omega t - \omega t - \theta) - \cos(\omega t + \omega t + \theta)]$$

$$= \frac{1}{2} [\cos(-\theta) - \cos(2\omega t + \theta)]$$
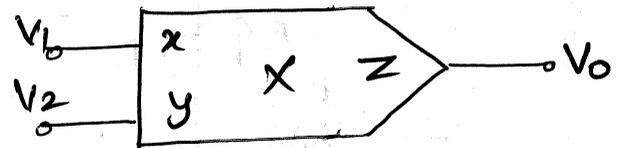
$$= \frac{1}{2} [\cos \theta - \cos(2\omega t + \theta)]$$



The dc term in the output is $V_o = \frac{V_x V_y}{V_{ref}} \frac{1}{2} \cos \theta$

The output voltage is proportional to phase difference θ .

EXPLAIN IN DETAIL ABOUT ANALOG MULTIPLIER USING EMITTER COUPLED TRANSISTOR PAIR:

* simple modulator using differential amplifier

* It can be used as a multiplier

* It has two transistors Q_1 and Q_2 act as a differential amplifier.

* input V_1 is given to differential amplifier ckt.

* The input signal V_2 is given to emitter coupled differential pair through constant current source.

* This multiplier circuit provides the output at two quadrant only.

$$I_{C1} = \frac{I_{EE}}{1 + e^{-v_1/v_T}}$$

$$I_{C2} = \frac{I_{EE}}{1 + e^{v_1/v_T}}$$

$v_T \rightarrow$ Thermal voltage

$$\Delta I_C = I_{C1} - I_{C2}$$

$$= \frac{I_{EE}}{1 + e^{-v_1/v_T}} - \frac{I_{EE}}{1 + e^{v_1/v_T}}$$

$$= I_{EE} \left[\frac{1}{1 + e^{-v_1/v_T}} - \frac{1}{1 + e^{v_1/v_T}} \right]$$

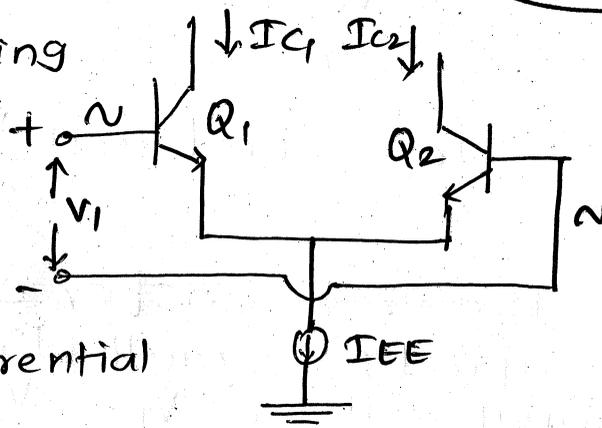


FIG: EMITTER COUPLED TRANSISTOR PAIR

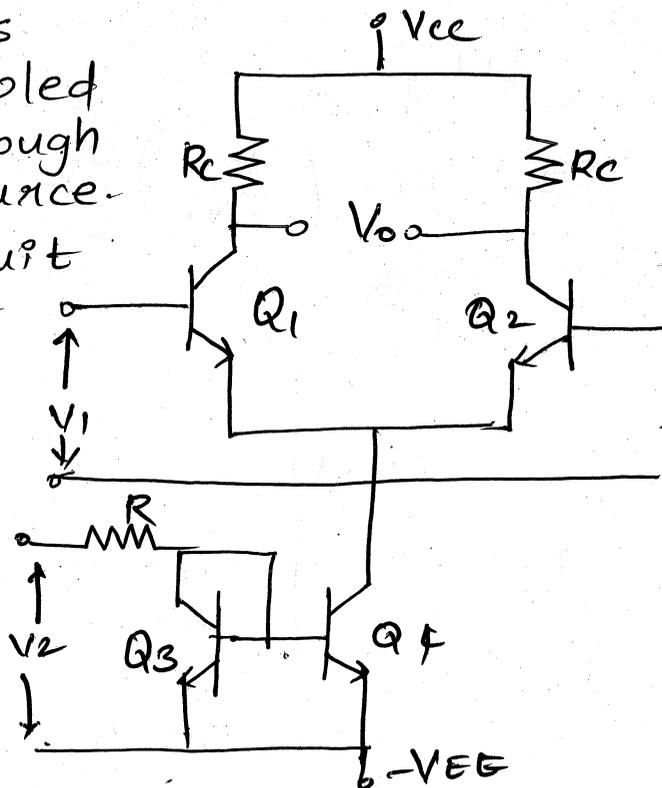


FIG: SIMPLE MODULATOR TYPE MULTIPLIER

$$\text{Note: } \frac{1}{1+e^{-x}} - \frac{1}{1+e^x} = \tanh\left(\frac{x}{2}\right)$$

$$\therefore x = \frac{V_i}{V_T}$$

$$\Delta I_C = I_{EE} \tanh \frac{V_i}{2V_T}$$

The dc transfer characteristics of emitter coupled pair multiplier. when the differential input voltage $V_i \ll V_T$

$$\Delta I_C = I_{EE} \tanh \left(\frac{V_i}{2V_T} \right)$$

$$= I_{EE} \left(\frac{V_i}{2V_T} \right)$$

$$\Delta I_C = I_{EE} \left(\frac{V_i}{2V_T} \right)$$

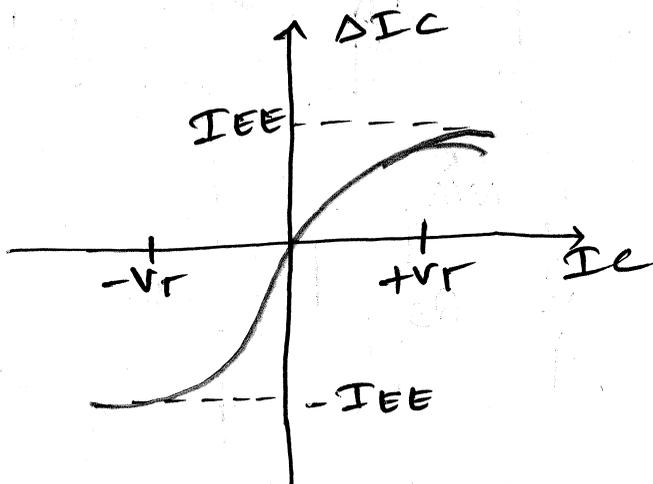


FIG. TRANSFER CHARACTERISTICS

GILBERT MULTIPLIER CELL:

* The Gilbert multiplier cell is a modification of the emittercoupled cell and allow this four quadrant multiplication.

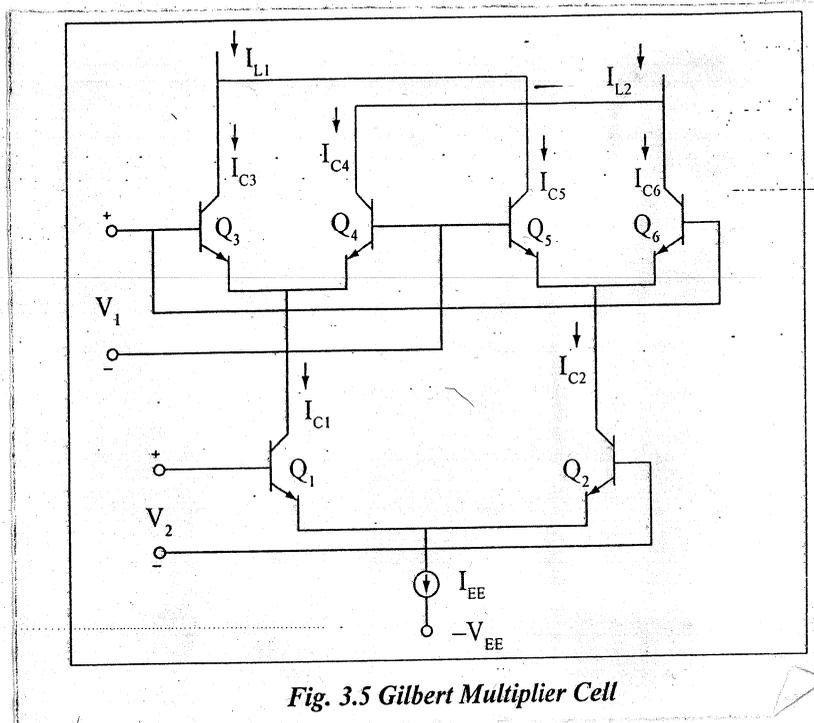


Fig. 3.5 Gilbert Multiplier Cell

ANALYSIS:

$$I_{C3} = \frac{I_{C1}}{1 + e^{-v_1/v_T}}, \quad I_{C4} = \frac{I_{C1}}{1 + e^{v_1/v_T}} \quad \text{--- (1)}$$

$$I_{C5} = \frac{I_{C2}}{1 + e^{v_1/v_T}}, \quad I_{C6} = \frac{I_{C2}}{1 + e^{-v_1/v_T}} \quad \text{--- (2)}$$

The collector currents I_{C1} and I_{C2}

$$I_{C1} = \frac{I_{EE}}{1 + e^{-v_2/v_T}}$$

$$I_{C2} = \frac{I_{EE}}{1 + e^{v_2/v_T}}$$

Substitute I_{C1} in I_{C3} and I_{C4}

$$I_{C3} = \frac{I_{EE}}{(1 + e^{-v_1/v_T})(1 + e^{-v_2/v_T})}$$

$$I_{C4} = \frac{I_{EE}}{(1 + e^{v_1/v_T})(1 + e^{-v_2/v_T})}$$

Substitute I_{C2} in I_{C5} and I_{C6}

$$I_{C5} = \frac{I_{EE}}{(1 + e^{+v_1/v_T})(1 + e^{+v_2/v_T})}$$

$$I_{C6} = \frac{I_{EE}}{(1 + e^{v_2/v_T})(1 + e^{-v_1/v_T})}$$

The differential output current $\Delta I = I_{L1} - I_{L2}$

$$I_{L1} = I_{C3} + I_{C5} ; \quad I_{L2} = I_{C4} + I_{C6}$$

$$\Delta I = (I_{C3} + I_{C5}) - (I_{C4} + I_{C6})$$

$$\Delta I = (I_{C3} - I_{C6}) - (I_{C4} - I_{C5})$$

$$\Delta I = I_{EE} \left[\tanh\left(\frac{v_1}{2v_T}\right) \tanh\left(\frac{v_2}{2v_T}\right) \right]$$

$$\begin{aligned} I_{C3} - I_{C6} &= \frac{I_{EE}}{(1 + e^{-v_1/v_T})(1 + e^{-v_2/v_T})} - \frac{I_{EE}}{(1 + e^{v_2/v_T})(1 + e^{-v_1/v_T})} \\ &= \frac{I_{EE}}{1 + e^{-v_1/v_T}} \left[\frac{1}{1 + e^{-v_2/v_T}} - \frac{1}{1 + e^{v_2/v_T}} \right] \end{aligned}$$

$$I_{C3} - I_{C6} = \frac{I_{EE}}{1 + e^{-v_1/v_T}} \tanh \frac{v_2}{2V_T}$$

$$I_{C4} - I_{C5} = \frac{I_{EE}}{(1 + e^{v_1/v_T})(1 + e^{-v_2/v_T})} - \frac{I_{EE}}{(1 + e^{v_1/v_T})(1 + e^{v_2/v_T})}$$

$$= \frac{I_{EE}}{1 + e^{v_1/v_T}} \left[\frac{1}{1 + e^{-v_2/v_T}} - \frac{1}{1 + e^{v_2/v_T}} \right]$$


$$I_{C4} - I_{C5} = \frac{I_{EE}}{1 + e^{v_1/v_T}} \tanh \frac{v_2}{2V_T}$$

$$\Delta I = \frac{I_{EE}}{1 + e^{-v_1/v_T}} \tanh \frac{v_2}{2V_T} - \frac{I_{EE}}{1 + e^{v_1/v_T}} \tanh \frac{v_2}{2V_T}$$

$$= I_{EE} \tanh \frac{v_2}{2V_T} \left[\frac{1}{1 + e^{-v_1/v_T}} - \frac{1}{1 + e^{v_1/v_T}} \right]$$

$$\Delta I = I_{EE} \tanh \left(\frac{v_2}{2V_T} \right) \tanh \left(\frac{v_1}{2V_T} \right)$$

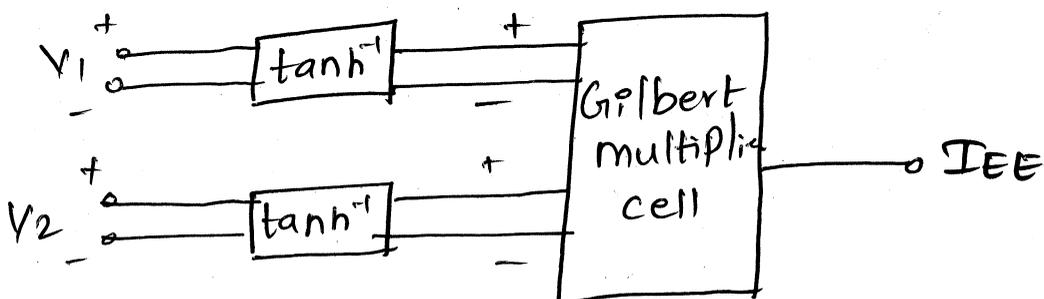
Gilbert multiplier cell with predistortion



APPLICATIONS:

- * Used in modulators in communication system
- * Used as phase detectors
- * Used as frequency doublers, square wave etc.

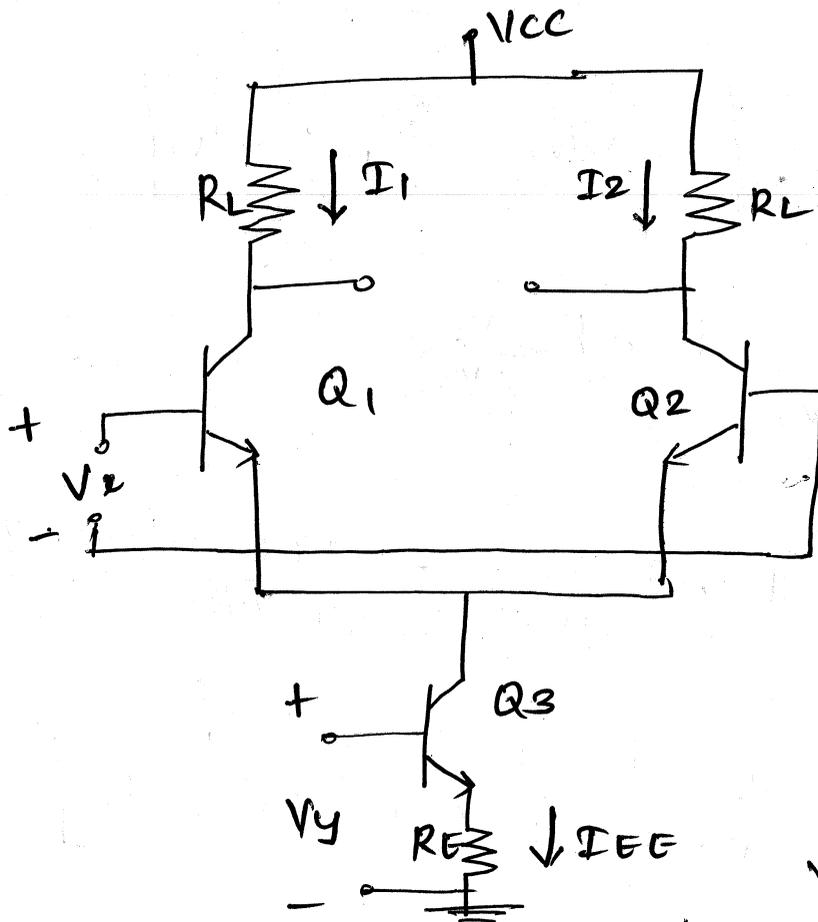VARIABLE TRANSCONDUCTANCE TECHNIQUE MULTIPLIERS:



* A simple differential circuit arrangement producing the principle of Variable Transconductance Technique multiplier.

The relationship between V_o and V_x

$$V_o = g_m R_L V_x$$

$$g_m = \frac{I_{EE}}{V_T}$$

Transconductance of stage

* V_y is input to the reference current source of the differential amplifier.

$$V_o = \frac{I_{EE}}{V_T} \cdot R_L \cdot V_x$$

$$= \frac{V_y}{V_T R_E} R_L V_x$$

$$V_o = V_x \cdot V_y \cdot \frac{R_L}{V_T R_E}$$

Note: $I = \frac{V}{R}$
 $I_{EE} = \frac{V_y}{R_E}$

Consider $\frac{R_L}{V_T R_E} = K$

$$V_o = K V_x V_y$$

$K \rightarrow$ scaling factor

EXPLAIN THE BASIC BLOCK DIAGRAM OF ADC and DAC?

- * Most of the real world physical quantities such as voltage, current, temperature, pressure are available in analog form.
- * Even though an analog signal represents a real physical parameter with accuracy.
- * For processing, transmission and storage purposes, it is often convenient to express these variables in digital form.
- * It gives better accuracy and reduces noise.
- * The operation of any digital communication is based upon analog to digital and digital to analog conversion.

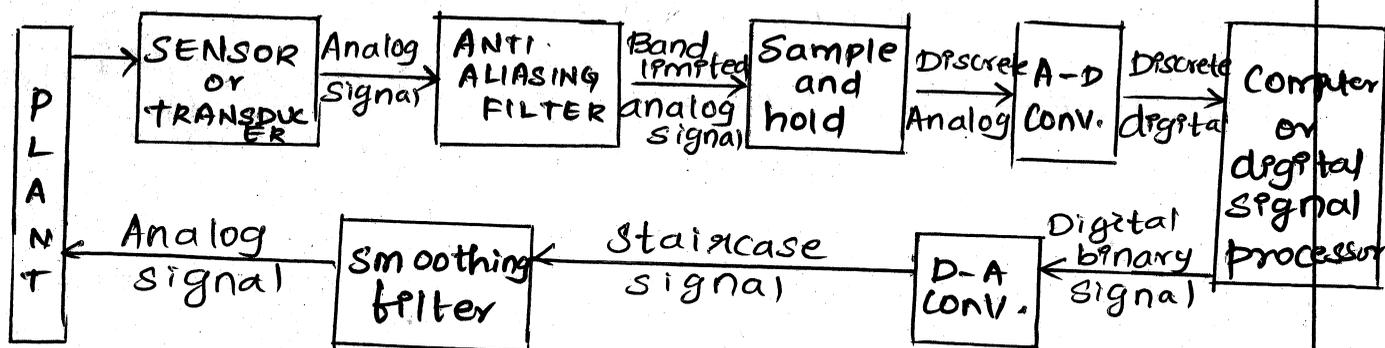


FIG: CIRCUIT SHOWING APPLICATION OF A/D and D/A CONVERTER

- * The analog signal obtained from the transducer is band limited by anti aliasing filter.
- * The signal is then sampled at a frequency rate more than twice the maximum frequency of the band limited signal.

* The sampled signal has to be held constant while conversion taking place in A/D converter.

* This requires that ADC should be preceded by a sample and hold circuit.

* The ADC output is a sequence in binary digit.

* The micro computer or digital signal processor performs the numerical calculations of the desired control algorithm.

* The D/A converter is to convert digital signal into analog and hence the function of DAC is exactly opposite to that of ADC.

* The D/A converter is usually operated at the same frequency as the ADC.

* The output of D/A converter is commonly a staircase.

* This staircase-like digital output is passed through the smoothing filter to reduce the effect of quantization noise.

* Both ADC and DAC are also known as data converters and are available in IC form.

* It may be mentioned here that for slowly varying signal, sometimes sample and hold circuit may be avoided without considerable error.

APPLICATIONS:

* Digital audio recording

* pulse code modulation transmission

* Data acquisition

* Digital multimeter

* Digital signal processing

* Microprocessor based Instrumentation.

EXPLAIN IN DETAIL ABOUT DAC TECHNIQUES AND ITS TYPES OF DAC?

* The input is an n -bit binary word D and is combined with a reference voltage V_R to give an analog output signal.

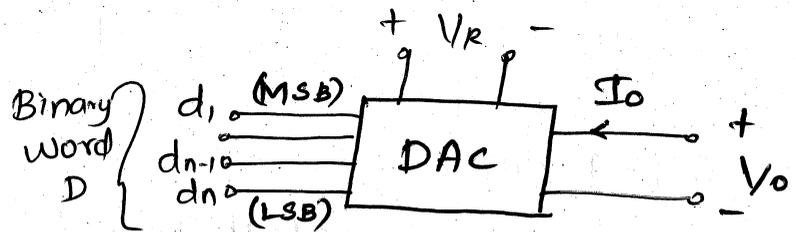


FIG: SCHEMATIC OF DAC

* The output of DAC can be either a voltage or current

* For a voltage output DAC, the D/A converter is mathematically described as

$$V_o = K V_{FS} (d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n})$$

V_o = Output Voltage

K = Scaling Factor usually adjusted to unity.

V_{FS} = Full Scale output Voltage.

d_1, d_2, \dots, d_n = n -bit binary word

d_1 = most significant bit with a weight of $V_{FS}/2$

d_n = Least significant bit with a weight of $V_{FS}/2^n$

TYPES OF DAC:


1. Weighted Resistor DAC
2. R-2R Ladder
3. Inverted R-2R Ladder

WEIGHTED RESISTOR DAC:

- * It uses a summing amplifier with a binary weighted resistor network.
- * It has n -electronics switches d_1, d_2, \dots, d_n controlled by binary input word.
- * These switches are single pole double throw (SPDT) type.
- * If the binary input to a particular switch is 1, it connects to the resistance of the reference voltage ($-V_R$).
- * If the input is 0, the switch connects resistor to the ground.
- * The output current I_0 for an ideal op-amp can be written as

$$I_0 = I_1 + I_2 + \dots + I_n$$
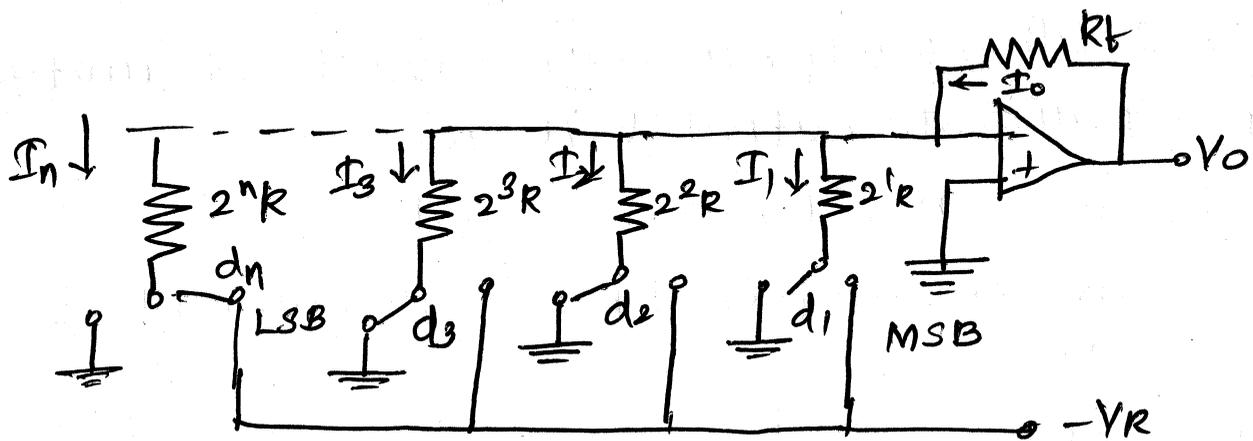
$$= \frac{V_R}{2^n R} d_1 + \frac{V_R}{2^{n-1} R} d_2 + \frac{V_R}{2^{n-2} R} d_3 + \dots + \frac{V_R}{2 R} d_n$$



A SIMPLE WEIGHTED RESISTOR DAC

$$= \frac{V_R}{R} (d_1 2^1 + d_2 2^2 + \dots + d_n 2^n)$$

The output voltage

$$V_o = I_0 R_f$$

$$= V_R \frac{R_f}{R} (d_1 2^1 + d_2 2^2 + \dots + d_n 2^n) \quad \text{--- (1)}$$

Basic DAC evaluation:

$$V_o = K V_{FS} (d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n}) \quad \text{--- (2)}$$

Comparing evaluation (1) and (2)

$R_f = R$ and then $K=1$ and $V_{FS} = V_R$

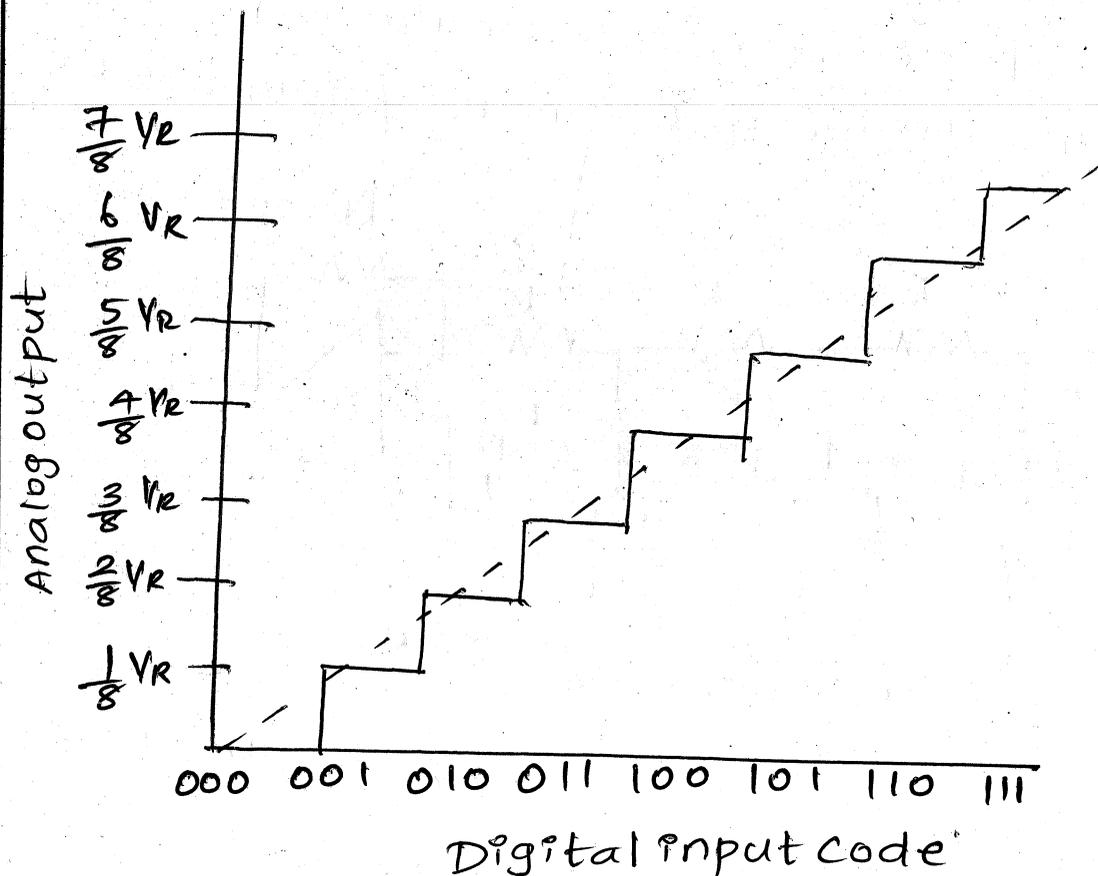


FIG. 1: TRANSFER CHARACTERISTICS OF A 3-BIT DAC

* The accuracy and stability of a DAC depends upon the accuracy of the resistors and the tracking of each other with temperature.

* One of the disadvantages of binary weighted type DAC is the wide range of resistor values required.

- * It may be observed that for better resolution, the binary word length has to be increased.
- * The switches are in series with resistors and therefore, their on resistance must be very low and they should have zero offset voltage.

R-2R LADDER DAC:

* Wide range of resistors are required in binary weighted resistor type DAC. This can be avoided by using R-2R Ladder type DAC where only two values of resistors are required.

* The typical value of R ranges from 2.5 kΩ to 10 kΩ.

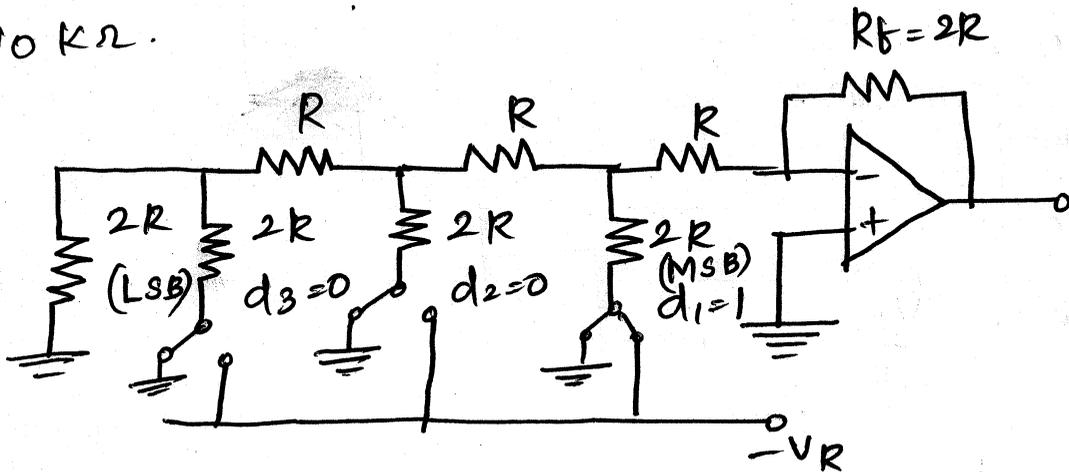


FIG: R-2R LADDER DAC

* Here the R-2R Ladder DAC is having 100 bit.

$$V_o = \left(-\frac{2R}{R} \right) \left(-\frac{V_R}{16} \right)$$

$$V_o = \frac{V_R}{8} = \frac{V_{FS}}{8}$$

$$\frac{-V_R \left(\frac{2}{3} R \right)}{2R + \frac{2}{3} R} = \frac{-V_R}{4}$$

$$V_o = -\frac{2R}{R} \left(\frac{-V_R}{4} \right)$$

$$= \frac{V_R}{2} = \frac{V_{FS}}{2}$$

output of 100-bit DAC

output of 100-bit DAC

INVERTED R-2R LADDER!



- * In weighted resistor type and R-2R ladder type DAC \rightarrow current flowing in the resistor changes as the input data changes
- * More power dissipation causes heating, which in turn creates non-linearity in DAC
- * This problem can be avoided by inverted R-2R Ladder DAC.
- * Position of MSB and LSB interchanged
- * Here each input binary word connects the corresponding switch either to ground or to the inverting input terminal of the op-amp which is also at virtual ground.
- * Since both the terminals of switches are at logical '0' \rightarrow The current flows through left on to the ground.
- * Logical '1' \rightarrow to the right, the current through 2R sinks to the virtual ground.
- * The circuit has the important property that the current divides equally at each of the nodes

$$I_1 = \frac{VR}{2R}; I_2 = \frac{VR/2}{2R} = \frac{I_1}{2^{n-1}}$$

$$I_3 = \frac{VR/4}{2R} = \frac{I_1}{4}; \text{ general; } I_n = \frac{I_1}{2^{n-1}}$$


$$V_o = I_o R = -R [I_1 + I_2 + I_3]$$

$$V_o = -R \left[I_1 + \frac{I_1}{2} + \frac{I_1}{4} \right]$$

$$= -R \left[\frac{V_R}{2R} d_1 + \frac{V_R}{4R} d_2 + \frac{V_R}{8R} d_3 \right]$$

$$= -R \frac{V_R}{R} \left[d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} \right]$$
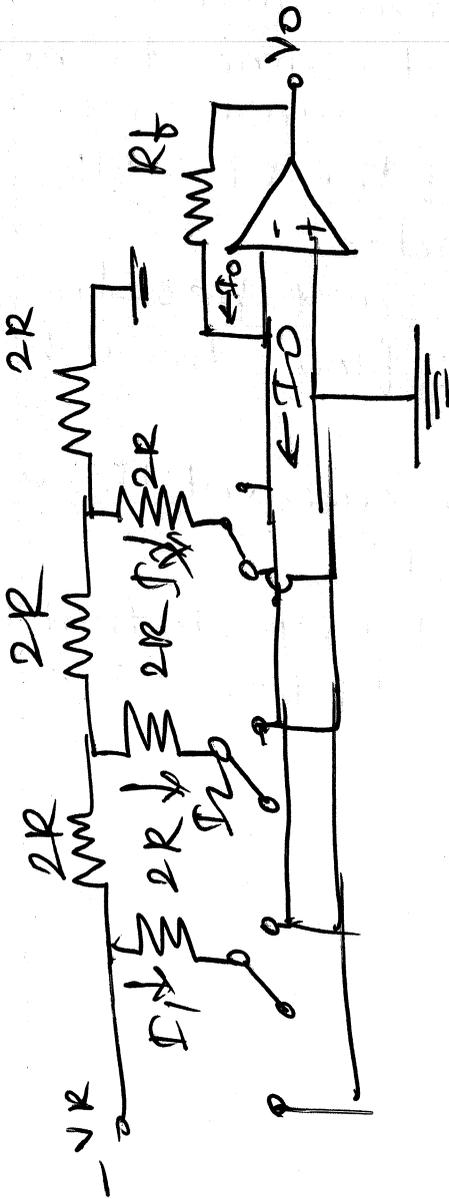
$$V_o = -V_R \left[d_1 2^{-1} + d_2 2^{-2} + d_3 2^{-3} \right]$$




(a) INVERTED R-2R
LADDER DAC

ANALOG TO DIGITAL CONVERTERS :

* The ADC is used for the purpose of converting analog to digital.

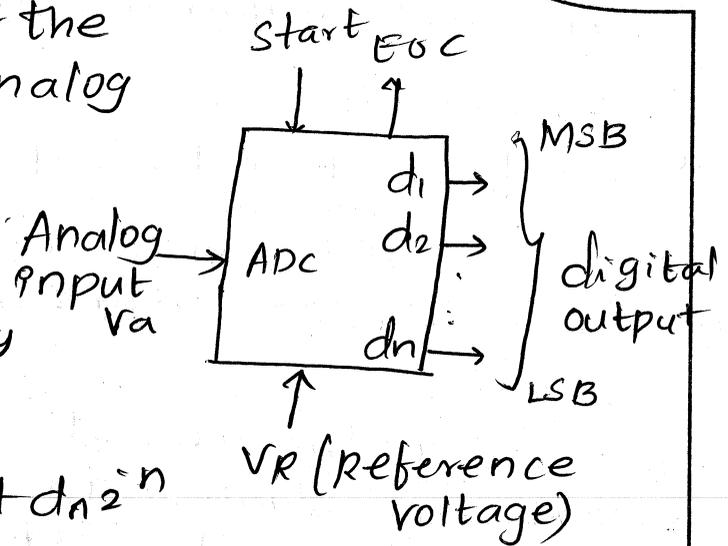* It accepts an analog input voltage V_a and produces binary d_1, d_2, \dots, d_n .




$$D = d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n}$$

$d_1 \rightarrow$ Most significant bit (MSB)

$d_n \rightarrow$ Least significant bit (LSB)

* ADC has two additional control lines START input to tell the ADC where to start conversion and EOC to announce when conversion is complete.

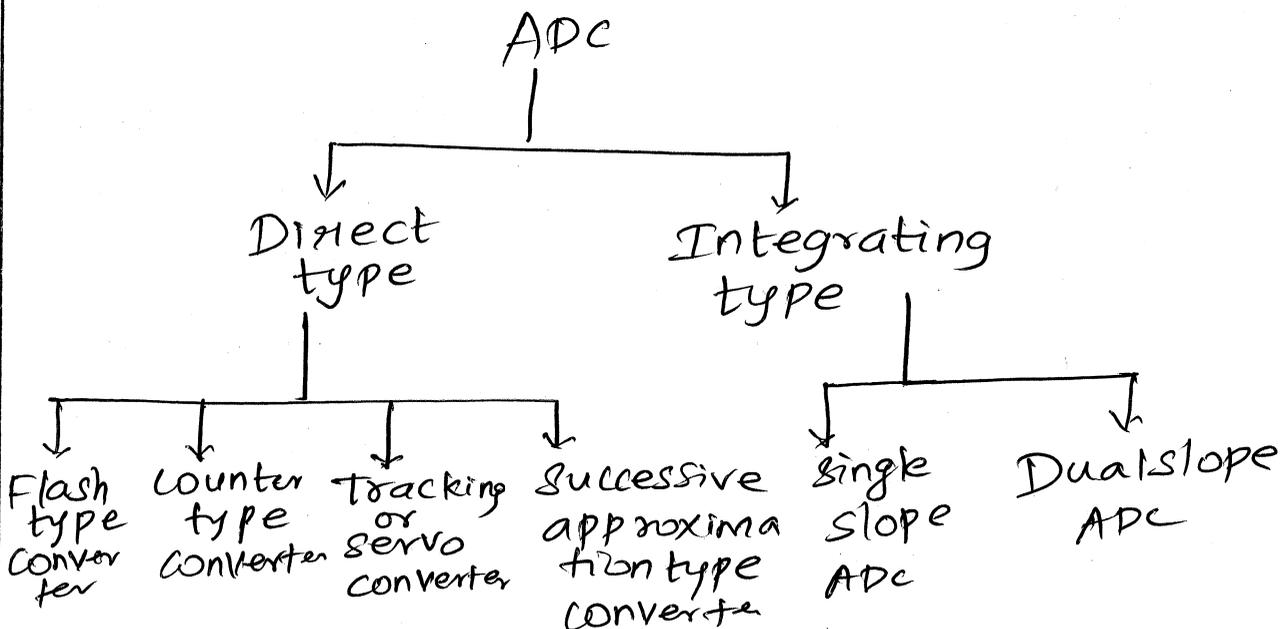* Dependent on the type of application ADCs are designed for microprocessor interfacing or to directly drive LCD or LED display.



(i) PARALLEL COMPARATOR (OR) FLASH TYPE ADC CONVERTER

* This type of ADC is also called simultaneous type or parallel comparator ADC.

→ Simplest ADC

→ fastest and most expensive


* The circuit consists of resistive divider network, 8 op-amp comparators and 8 to 3 line priority encoder.

* Since all the resistors in resistive divider network are equal, so the voltage levels at the nodes are equally divided between V_R to ground.

* The comparator compares the analog input voltage V_a with each of the node voltage and produce the output.

* The circuit consists of $2^n - 1$ comparators.

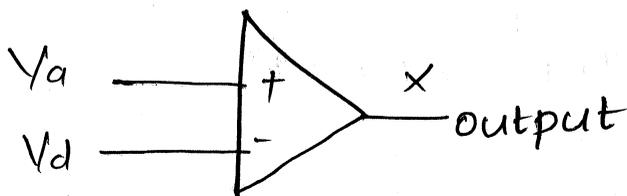* The analog input signal is applied to non-inverting terminal of all comparators and the comparative voltage is derived from reference voltage using potential divider rule.



Voltage input	Logical output
$V_a > V_d$	$X = 1$
$V_a < V_d$	$X = 0$
$V_a = V_d$	previous value

* In the basic comparator, if input V_a greater than potential divider voltage (or) reference voltage of that comparator ($V_a < V_d$). The output is equal to 1. If V_a is less than reference voltage ($V_a < V_d$), the output is 0.

Truth table:


Input voltage V_a	X_7	X_6	X_5	X_4	X_3	X_2	X_1	X_0	Y_2	Y_1	Y_0
0 to $V_R/8$	0	0	0	0	0	0	0	1	0	0	0
$V_R/8$ to $2V_R/8$	0	0	0	0	0	0	1	1	0	0	1
$2V_R/8$ to $3V_R/8$	0	0	0	0	0	1	1	1	0	1	0
$3V_R/8$ to $4V_R/8$	0	0	0	0	1	1	1	1	0	1	1
$4V_R/8$ to $5V_R/8$	0	0	0	1	1	1	1	1	1	0	0
$5V_R/8$ to $6V_R/8$	0	0	1	1	1	1	1	1	1	0	1
$6V_R/8$ to $7V_R/8$	0	1	1	1	1	1	1	1	1	1	0
$7V_R/8$ to V_R	1	1	1	1	1	1	1	1	1	1	1

TRUTH TABLE FOR 3 BIT FLASH TYPE A/D CONVERTER

DISADVANTAGE:

- * $2^n - 1$ comparators need.
- * The number of comparators doubles for each added bit. A 2-bit adc requires 3 comparators while for 3-bit ADC requires 7 comparators; approximately doubles for each added bit.

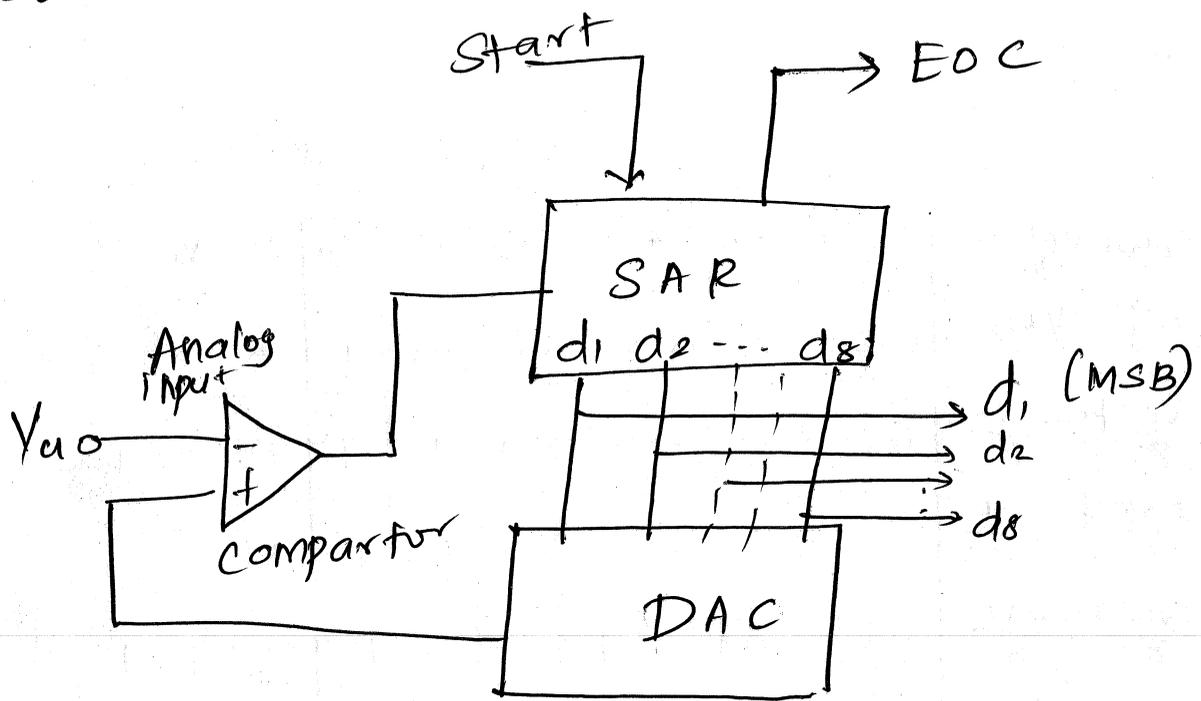SUCCESSIVE APPROXIMATION TYPE A/D CONVERTER



SUCCESSIVE APPROXIMATION TYPE DAC

- * The successive approximation technique complete n -bit conversion in just n -clock periods.
- * An eight bit A/D converter would require 8 clock pulses to obtain digital output.
- * SAR is successive approximation register to find the required value of each bit by trial and error.
- * With the arrival of start command, the SAR sets the MSB, $d_1 = 1$ with all other bits to zero, so that trial code is 1000000. The output V_d of DAC is now compared with analog input V_a .
- * If $V_a > V_d$, then 10000000 is less than the correct digital representation. The MSB is left at 1 and the next lower significant bit is made 1 and further tested.

* If V_a less than the DAC output, then 10000000 is greater than the correct digital representation. MSB to 0 and go on to the next lower significant bit.

* It required 8 clock pulses to produce the correct digital output of the analog input additional clock pulse is used to load the o/p resistor and reinitialize the circuit

Correct digital representation	V_d at different stage of conversion	Comparator output
11010100	10000000	1 (initial output)
	11000000	1
	11100000	0
	11010000	1
	11011000	0
	11010100	1
	11010110	0
	11010101	0
	11010100	

* The drawback of this technique is slow speed, the number of clock pulses equal to number of conversions 8-clock cycles need to convert 3 bit A/D.

The first part of the document discusses the importance of maintaining accurate records of all transactions. It emphasizes that every entry should be supported by a valid receipt or invoice. The second part outlines the procedures for handling discrepancies and errors, including the steps to be taken when a mistake is identified. The final section provides a summary of the key points and offers advice on how to ensure the highest level of accuracy and transparency in all financial reporting.

The following table provides a detailed breakdown of the data collected during the reporting period. Each row represents a different category, and the columns show the corresponding values for each metric.

Category	Value 1	Value 2	Value 3
Category A	1000	2000	3000
Category B	1500	2500	3500
Category C	2000	3000	4000
Category D	2500	3500	4500
Category E	3000	4000	5000
Category F	3500	4500	5500
Category G	4000	5000	6000
Category H	4500	5500	6500
Category I	5000	6000	7000
Category J	5500	6500	7500

The data presented in the table above shows a clear upward trend across all categories. This indicates that the overall performance has improved significantly over the period. The consistent growth in each category suggests that the implemented strategies are effective and sustainable. It is important to continue monitoring these trends and to make adjustments as needed to maintain this positive trajectory. The final section of the report provides a comprehensive overview of the findings and offers recommendations for future actions.