


IIIRD YEAR

EEE

EE8451 - LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

UNIT-IV

APPLICATION IC'S

 

IC 723 GENERAL PURPOSE REGULATOR:



* In three terminal fixed Voltage regulators have the following limitations.

1. No short circuit protection
2. output voltage is fixed

* The limitation have been overcome in the 723 general purpose regulators.

* The zener diode, a constant current source and reference amplifier produce a fixed voltage of about 7 Volts at the terminal V_{ref} .

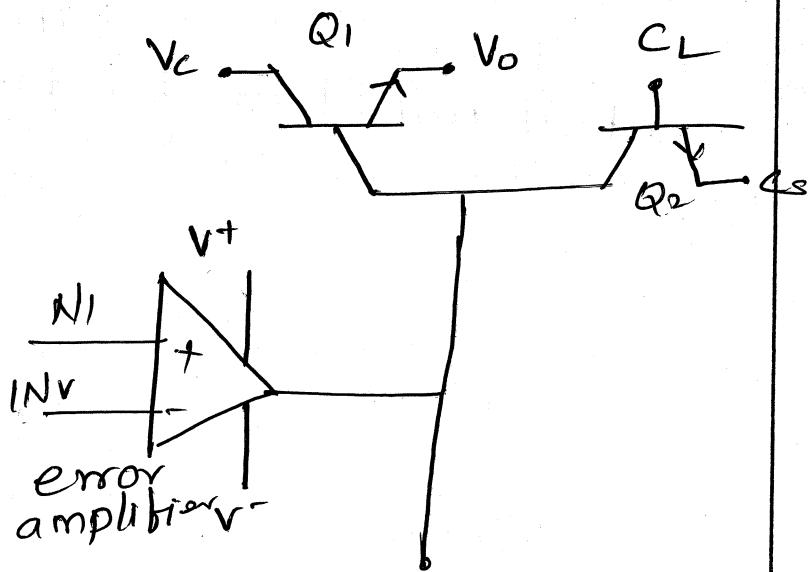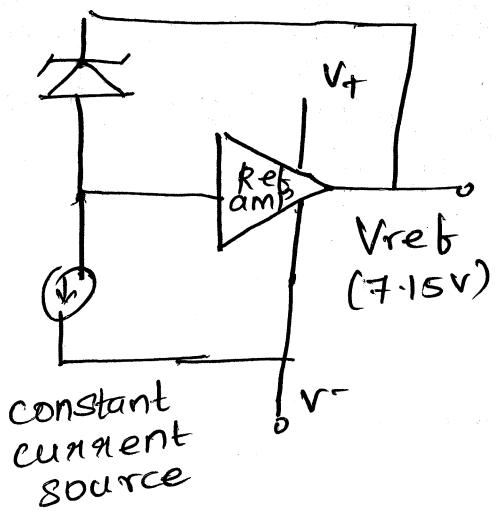* The constant current source forces the zener to operate at a fixed point so that the zener outputs a fixed voltage.




- * The power transistor Q_1 is in series with unregulated power supply V_{in} and regulated output voltage V_o . So it must absorb the difference between these two voltages whenever any fluctuation in output voltage V_o occurs.

- * The transistor Q₁ is also connected as an emitter follower and therefore provides sufficient current gain to drive the load.
- * The output voltage is sampled by R₁-R₂ divide and fed back to the (-) input terminal of the op-amp error amplifier.
- * This sampled voltage is compared with the V_{ref}. The output V_O of the error amplifier drives the series transistor Q₁.
- * If output voltage increases (i.e. due to variation in load current), the sampled voltage βV_O also increases.

$$\beta = \frac{R_2}{R_1 + R_2}$$

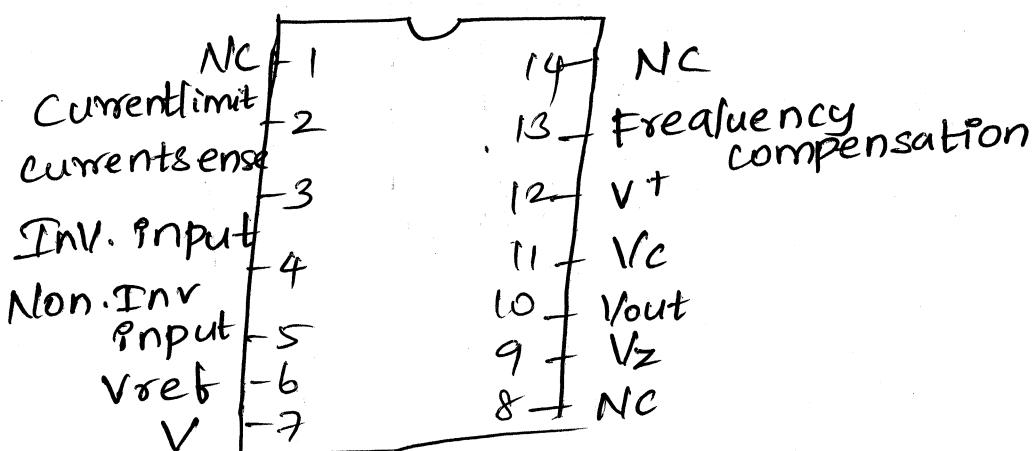- * In turn reduces output voltage V_O of diff-erential amplifier due to 180° phase difference provided by OP-AMP. V_O is applied to base of Q₁, which is used as an emitter follower.



PIN DETAIL OF IC723

A voltage regulator is an electronic circuit that provides a dc voltage independent of load current, temperature and ac line voltage variations.

The circuit consist of 4 parts

1. Reference voltage circuit
2. Error amplifier
3. Series pass transistor
4. Feedback network


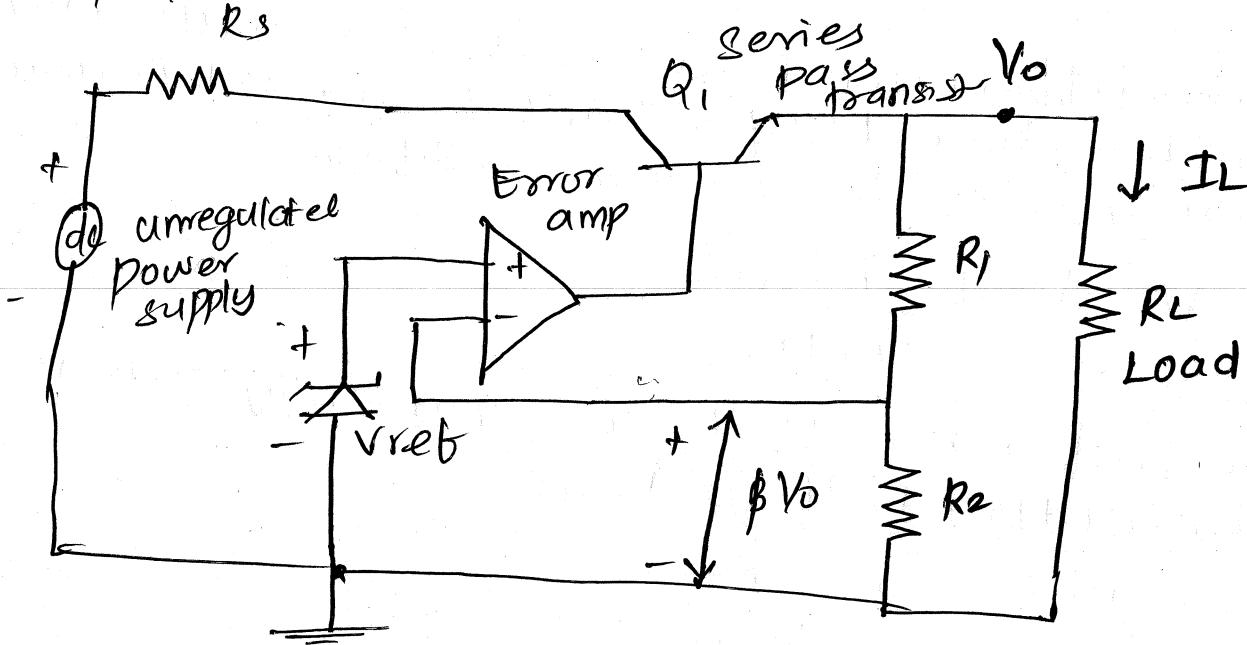


FIG: SERIES REGULATOR'S

MODES OF IC 723 REGULATOR

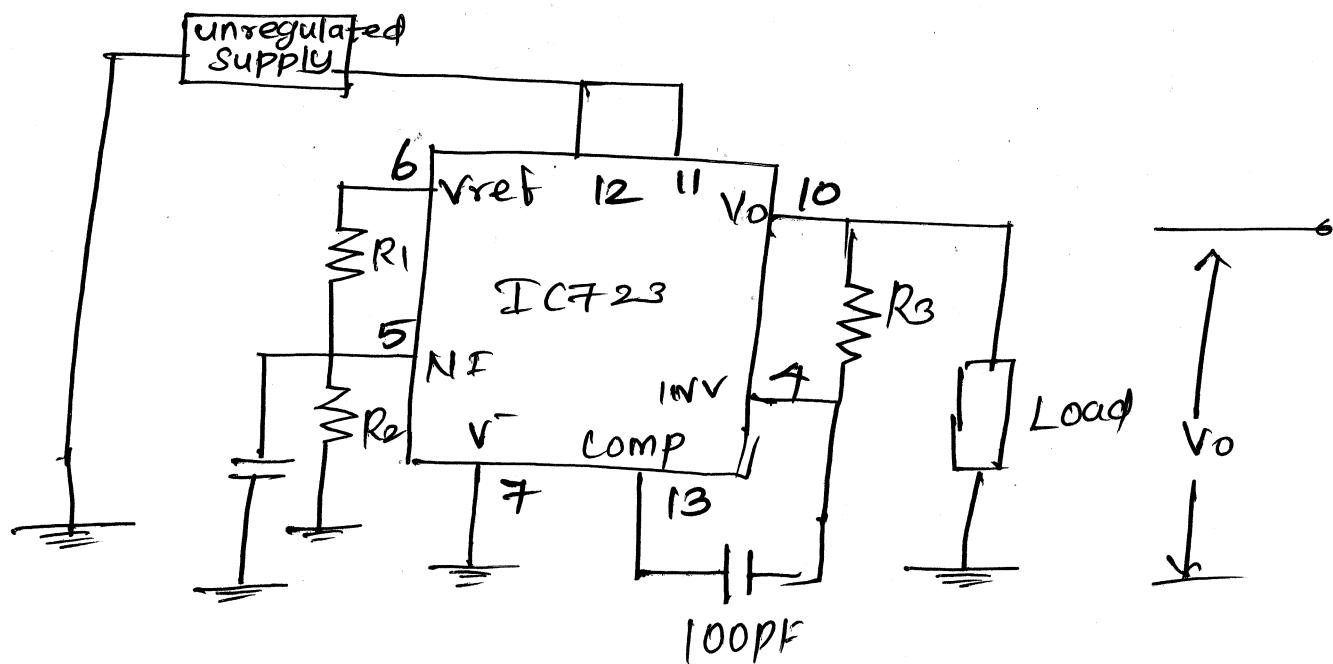

LOW POWER REGULATOR USING IC 723

* A simple positive low voltage regulator (2v to 7V).

* The voltage at NI terminal of the error amplifier - due to $R_1 R_2$ divider is

$$V_{NI} = V_{ref} = \frac{R_2}{R_1 + R_2}$$


* The difference between V_{NI} and output voltage V_o which is directly fed back to the INV terminal is amplified by the error amplifier

$$V_o = V_{ref} \frac{R_2}{R_1 + R_2}$$

The reference voltage is typically 7.15 V. So the output voltage V_o is

$$V_o = 7.15 \times \frac{R_2}{R_1 + R_2}$$

HIGH VOLTAGE REGULATOR USING IC 723

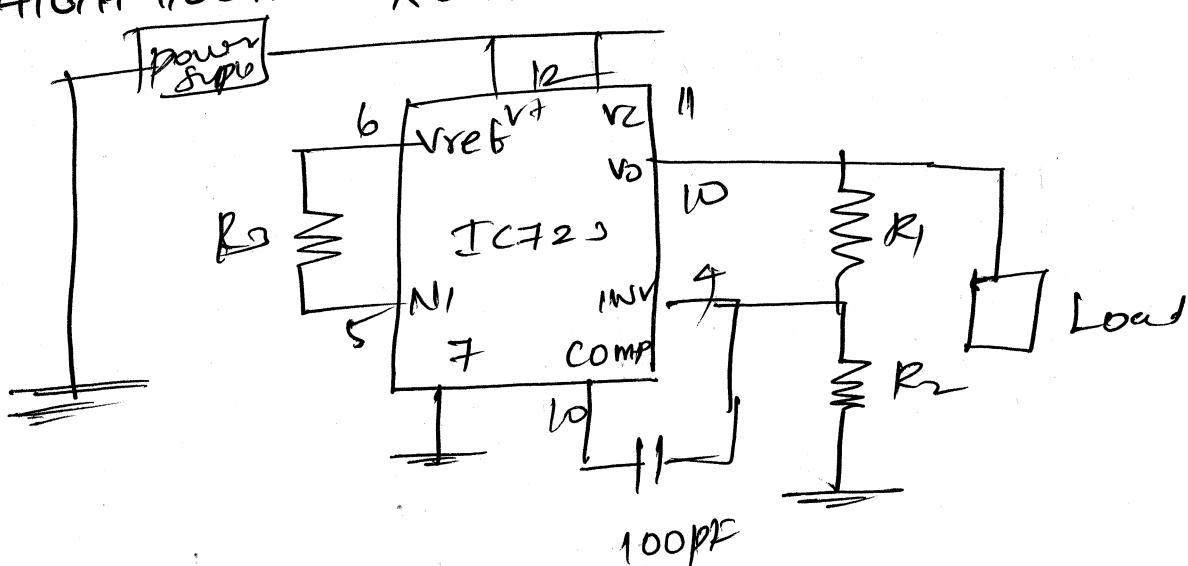

* The circuit produces regulator output voltage greater than 7V. The NI terminal connects directly to Vref through R_3 .


$$Av = 1 + \frac{R_1}{R_2}$$

$$V_o = V_{ref} \left(1 + \frac{R_1}{R_2} \right)$$

$$V_o = 7.15 \left(1 + \frac{R_1}{R_2} \right)$$

ICL 8038 FUNCTION GENERATOR:

- * Function generators are designed to provide the basic waveforms such as Square Wave, triangular Wave and Sine wave.
- * They are also called as waveform generators.
- * The operation of ICL 8038 is based on charging and discharging of a grounded capacitor C , whose charging and discharging rates are controlled by programmable current generators I_A and I_B respectively.
- * When switch is at position A, the capacitor charges at a rate determined by current source I_A .
- * Once the capacitor voltage reaches the threshold value V_{OT} switch position to change from position A to B.

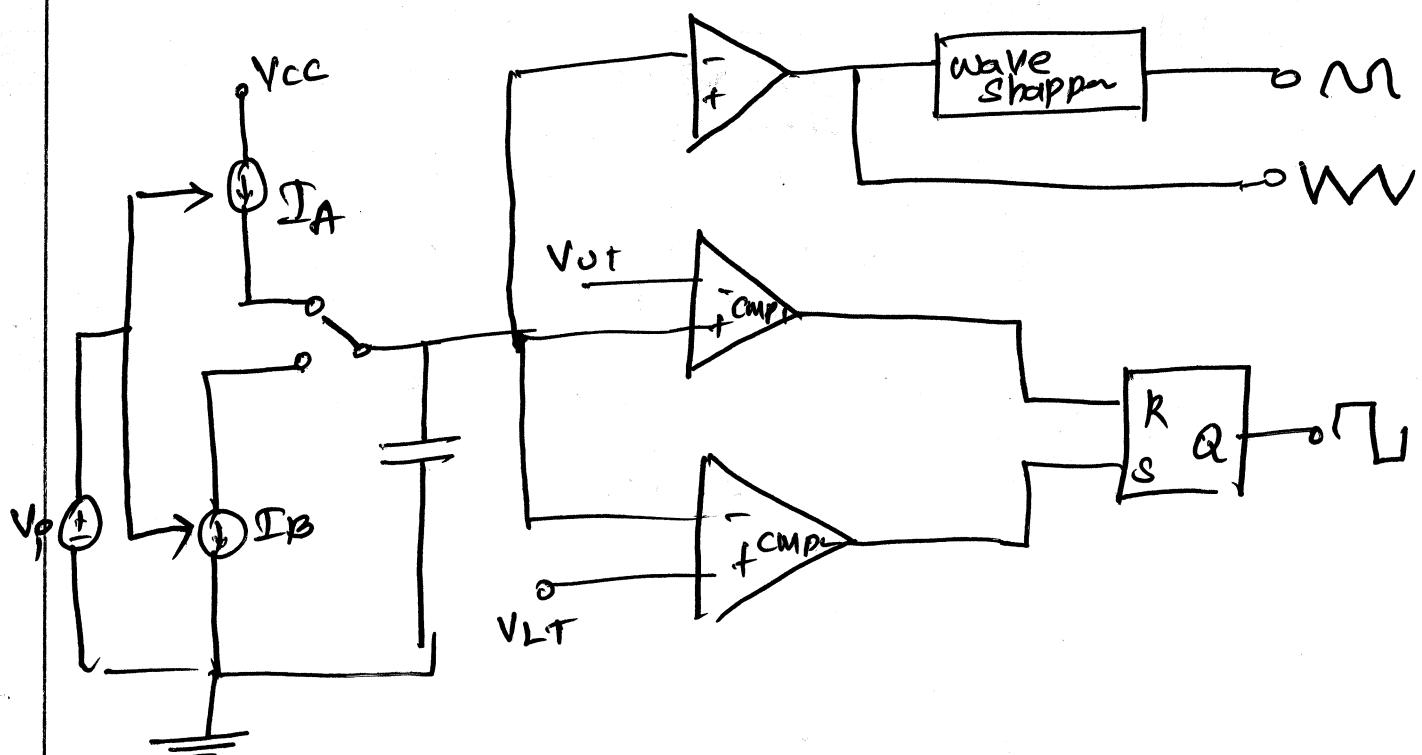

BLOCK DIAGRAM OF ICL 8038
FUNCTION GENERATOR

FREQUENCY OF OUTPUT WAVEFORM:

$$f_{out} = \frac{1}{T}$$

$$T = T_C + T_D$$

$$T_C = \Delta V_C \times \frac{1}{\text{charging current}} \times C$$

$$I = \frac{V}{R}$$

$$T_C = \frac{V_{CC}}{3} \times \frac{R_A}{V_i} \times C$$

$$T_C = \frac{R_A C V_{CC}}{3 V_i}$$

The discharging time T_D can be given as

$$T_D = \Delta V \times \frac{1}{\text{discharging current}} \times C$$

$$= \frac{V_{CC}}{3} \times \frac{1}{\left(\frac{2V_i - V_o}{R_B} - \frac{V_o}{R_A} \right)} \times C$$

$$= \frac{V_{CC}}{3} \times \frac{1}{\frac{2V_i R_A - V_o R_B}{R_A R_B}} \times C$$

$$= \frac{V_{CC} \times R_A R_B \times C}{3 (2V_i R_A - V_o R_B)}$$

$$= \frac{V_{CC}}{3 V_i} \times \frac{R_A R_B \times C}{(2R_A - R_B)}$$

$$T_d = \frac{C R_A V_{CC}}{3V_i} \left(\frac{R_B}{2R_A - R_B} \right)$$

$$T = T_c + T_d$$

$$= \frac{C R_A V_{CE}}{3V_i} + \frac{C R_A V_{CE}}{3V_i} \left(\frac{R_B}{2R_A - R_B} \right)$$

$$= \frac{C R_A V_{CC}}{3V_i} \left[1 + \frac{R_B}{2R_A - R_B} \right]$$

$$= \frac{C R_A V_{CC}}{3V_i} \left[\frac{2R_A - R_B + R_B}{2R_A - R_B} \right]$$

$$T = \frac{R_A C V_{CC}}{3V_i} \left[\frac{2R_A}{2R_A - R_B} \right]$$

$$f_{out} = \frac{1}{T}$$

$$= \frac{3V_i}{R_A C V_{CC}} \left(\frac{2R_A - R_B}{2R_A} \right)$$

Duty cycle is given as

$$\% d = \frac{T_c}{T_c + T_d} \times 100$$

$$= \frac{C R_A V_{CC}}{3V_i} \times 100$$

$$\frac{C R_A V_{CC}}{3V_i} + \frac{C R_A V_{CC}}{3V_i} \left(\frac{R_B}{2R_A - R_B} \right)$$

$$= \frac{C R_A V_{CC}}{3V_i} \left(1 + \frac{R_B}{2R_A - R_B} \right)$$

$$= \frac{1}{\frac{2R_A - R_B + R_D}{2R_A - R_B}}$$

$$= \frac{2R_A - R_B}{2R_A} \times 100$$

$$q_o d = \left(1 - \frac{R_B}{2R_A} \right) \times 100$$

Specifications:

Supply Voltage: $\pm 18V$ or $36V$

Power dissipation: $750mW$

Input Voltage: max of supply voltage level

Input Current: $25mA$

Output sink current : $25mA$

Storage temperature range: $65^\circ C$ to $125^\circ C$

Distortion: 1%

Linearity: 0.1%

| | |
|----|------------------------------|
| 1 | NC |
| 13 | NC |
| 12 | Sine adjust |
| 11 | VEE or GND |
| 10 | TPM ^{ing} capacitor |
| 9 | Squareout |
| 8 | DFMSweep out |
| 7 | FMBias |
| 6 | V _{CC} |
| 5 | freq adjust |
| 4 | Duty cycle |
| 3 | Triangle out |
| 2 | Sine out |
| 1 | Sine adjust |

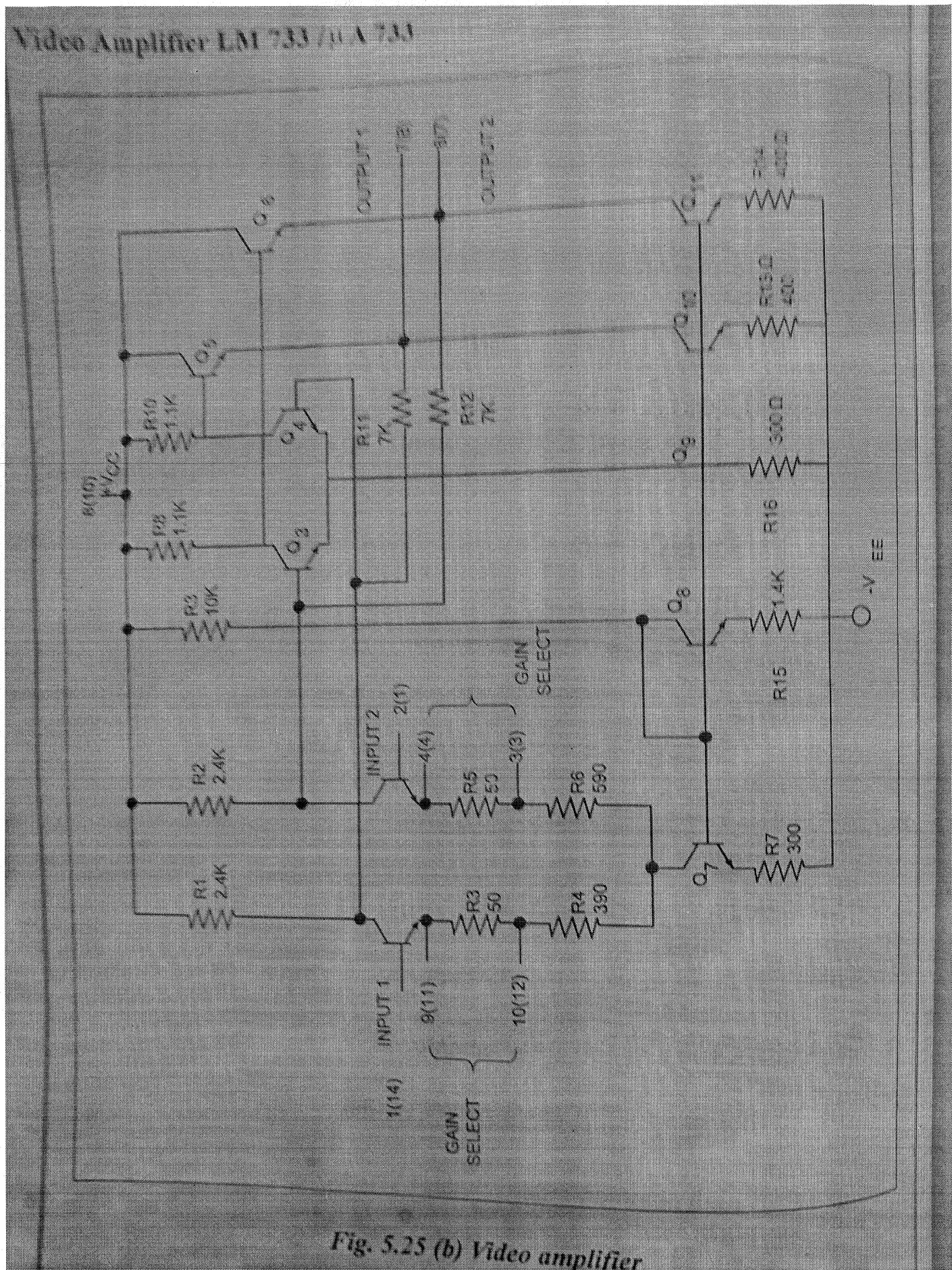


Fig. 5.25 (b) Video amplifier


VIDEO AMPLIFIER: LM 733 IC



- * It consists of a two stage differential input, differential output and wideband Video amplifier.
- * The internal series-shunt feedback width with low phase distortion and high gain stability.
- * The emitter follower output provides a high current drive and low impedance.

FEATURES:

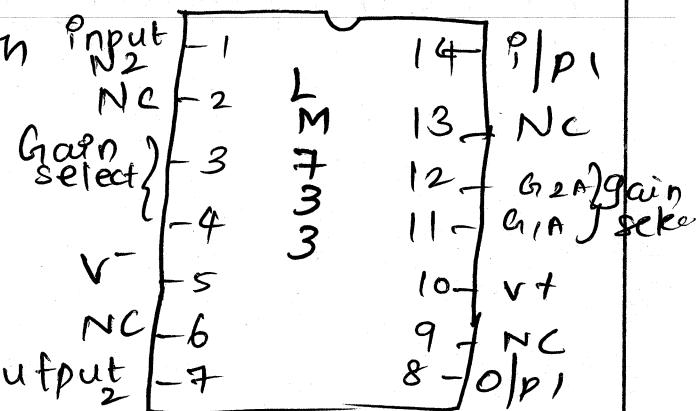- * It has wide band width of 120 MHz.
- * It offers an input resistance of $250\text{ k}\Omega$.
- * Gains 10, 100 and 400 are selectable.
- * External frequency compensation not required.
- * It provides high CMRR.



PIN DIAGRAM
OF LM 733

OPERATION:

- * It consists of two cascaded BJT differential amplifier stage and a balanced emitter follower stage.
- * The wideband width is achieved by a value of load resistance for the two differential amplifier stage.
- * The input stage comprises Q₁, Q₂ and the load resistors R₁ and R₂. The transistor Q₇ provides current sink biasing for the first differential stage.
- * The second stage formed by Q₃ and Q₄ driver by balanced output available from

the first stage resistors R_9 and R_{10} act as load for differential stage.

- * The balanced output from the second stage drive to emitter follower stage realized by Q_5 and Q_6 respectively Q_{10} and Q_{11} acts as current sink bias for the emitter followers.
- * Resistor Q_{11} and Q_{12} provide the negative feedback from the output terminals of the second stage.
- * The diode connected transistor Q_8 along with R_8 and R_{15} provides the overall biasing for the circuit by driving the current sink biasing.

AUDIO POWER AMPLIFIER: LM 380



- * The small signal amplifiers are voltage amplifiers and the large signal power amplifier supply a large signal current to load such as speakers and motors.
- * The monolithic power transistors used in audio power amplifiers.

FEATURES:

- * Voltage range: 5V to 20V
- * Operates with low quiescent power gain
- * Voltage range of 34 dB can be achieved
- * It can deliver high peak current of 1.3 A max
- * High input impedance
- * Low distortion.

Functional diagram description:

The internal schematic consists of four stages

(i) PNP emitter follower

(ii) Differential amplifier

(iii) Common emitter

(iv) Quasi complementary emitter follower

* Transistor Q₁ and Q₂ forms first PNP emitter follower input stage

* Output drives Q₃ - Q₄ PNP differential pair

* Q₅ and Q₆ act as collector load for PNP differential pair

* The transistor Q₇ and Q₈ form current mirror and thus establish collector current of Q₅

- * The transistor Q9 forms common emitter amplifier Stage
- * The capacitor C connected between base and collector Q9 provides the internal compensation
- * Q10 and Q12 produce a quasi complementary emitter follower stage

PIN DIAGRAM

