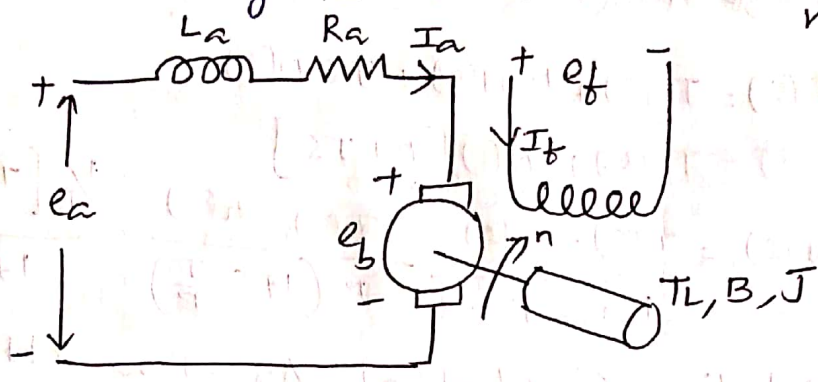




1. Transfer Function of DC Motor & Load!


In Separately Excited DC Motor with Armature voltage control method, Field current is constant but armature voltage is varied.



neglect rotational speed

- e_a - Armature voltage
- R_a - Armature resistance
- e_b - back emf
- e_f - field voltage
- T - Motor torque
- J - Moment of Inertia
- L_a - Armature Inductance
- I_a - Armature Current
- I_f - Field Current
- n - motor Speed
- B - damping Co-efficient
- T_L - Torque Load

Electrical Analysis:

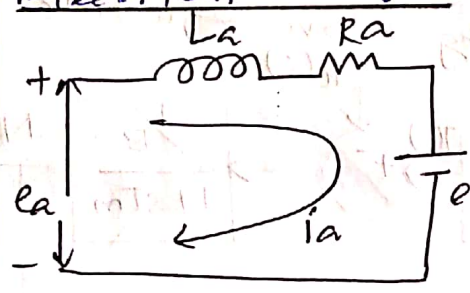


Applying KVL:

$$e_a = e_b + R_a i_a + L_a \frac{di_a}{dt}$$

$$e_b \propto \phi \frac{d\theta}{dt} \therefore \frac{d\theta}{dt} = n \quad \text{--- (1)}$$

$$e_b = k_a \phi n \quad \text{--- (2)}$$

Mechanical Analysis:

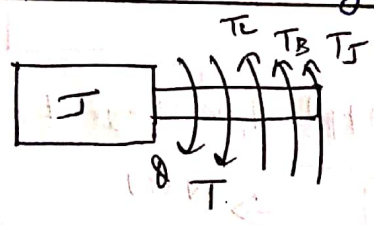

Applying Newton's law:

$$T = T_L + T_B + T_J$$

$$T = T_L + B \frac{d\theta}{dt} + J \frac{d^2\theta}{dt^2}$$

$$T = T_L + Bn + J \frac{dn}{dt} \quad \text{--- (3)}$$

$$T = k_a \phi I_a \quad \text{--- (4)}$$

Taking Laplace Transform from eq (1) to (4)

$$E_a(s) = E_b(s) + R_a I_a(s) + s L_a I_a(s) \quad \text{--- (5)}$$

$$E_b(s) = k_a \phi N(s) \quad \text{--- (6)}$$

$$T(s) = T_L(s) + B N(s) + J s N(s) \quad \text{--- (7)}$$

$$T(s) = k_a \phi I_a(s) \quad \text{--- (8)}$$

From equation (5)

$$E_a(s) = E_b(s) + R_a I_a(s) + s L_a I_a(s)$$

$$E_a(s) = E_b(s) + I_a(s) [R_a + sL_a]$$

$$I_a(s) = \frac{E_a(s) - E_b(s)}{R_a + sL_a} = \frac{E_a(s) - E_b(s)}{R_a (1 + s \frac{L_a}{R_a})} = \frac{1}{R_a} \frac{[E_a(s) - E_b(s)]}{1 + sT_a}$$

$T_a = \frac{L_a}{R_a}$ electrical time constant of the Armature ckt.

From equation (7)


$$T(s) = T_L(s) + B N(s) + J s N(s)$$

$$T(s) = T_L(s) + N(s) [B + J s]$$

$$N(s) = \frac{T(s) - T_L(s)}{B + sJ} = \frac{T(s) - T_L(s)}{B (1 + s \frac{J}{B})} = \frac{1}{B} \frac{[T(s) - T_L(s)]}{1 + sT_m}$$

$T_m = \frac{J}{B}$ mechanical time constant of Armature ckt.

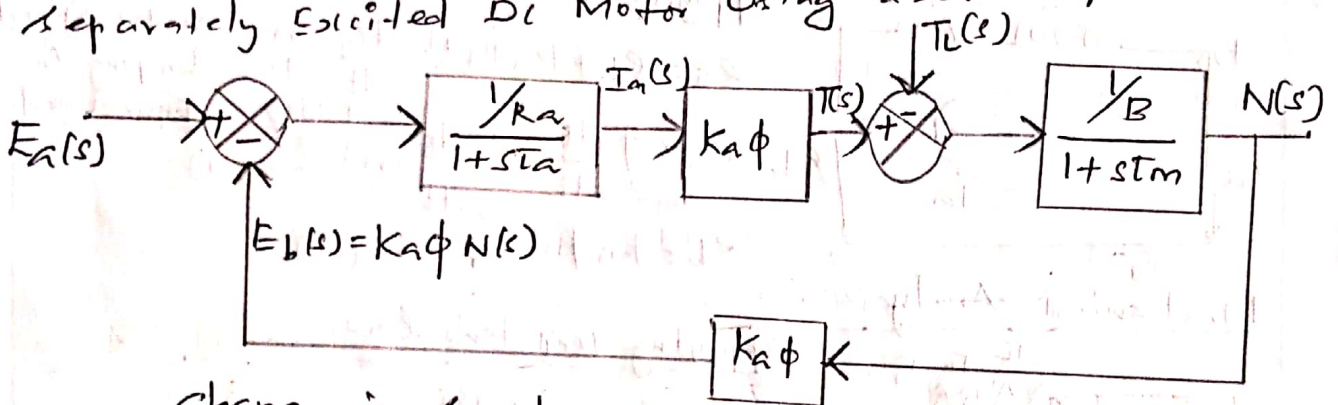To form feedback loop in the form of Back Emf is separately excited DC Motor using above equations.



change in speed $N(s)$ disturbs Applied Voltage $E_a(s)$ & $T_L(s)$

$N(s) = \text{block 1 transfer function} + \text{block 2 transfer function}$

$$\text{Block 1} = \frac{G_1(s)}{1 + G_1(s)H_1(s)} \cdot E_a(s), \quad \text{Block 2} = \frac{G_2(s)}{1 + G_2(s)H_2(s)} \cdot T_L(s)$$

$$\text{So } N(s) = \frac{G_1(s)}{1 + G_1(s)H_1(s)} \cdot E_a(s) + \frac{G_2(s)}{1 + G_2(s)H_2(s)} \cdot T_L(s)$$


Where;

$$G_1(s) = \frac{1/R_a}{1 + sT_a} (K_a \phi) \frac{1}{B} \frac{1}{1 + sT_m}$$

$$H_1(s) = K_a \phi$$

$$G_2(s) = \frac{-(1/B)}{1 + sT_m}, \quad H_2(s) = \frac{-(K_a \phi)^2 / R_a}{1 + sT_a}$$

Now neglecting the load torque T_L

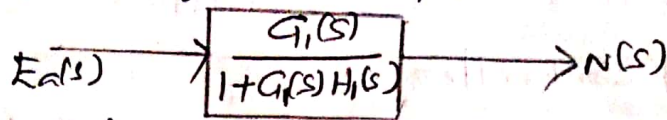

$$\frac{N(s)}{E_a(s)} = \frac{(K_a \phi) / R_a B}{1 + \frac{(K_a \phi) / R_a B}{(1+sT_a)(1+sT_m)}} = \frac{(K_a \phi) / R_a B}{(1+sT_a)(1+sT_m) + (K_a \phi)^2 / R_a B}$$

$$\frac{N(s)}{E_a(s)} = \frac{K_a \phi}{R_a B (1+sT_a)(1+sT_m) + (K_a \phi)^2}, \text{ If } T_a \ll T_m, T_a \text{ neglected}$$


$$\frac{N(s)}{E_a(s)} = \frac{K_a \phi}{R_a B (1+sT_m) + (K_a \phi)^2} = \frac{K_a \phi}{R_a B + R_a B s T_m + (K_a \phi)^2}$$

Dividing $R_a B + (K_a \phi)^2$ in all terms

$$\frac{N(s)}{E_a(s)} = \frac{K_a \phi / R_a B + (K_a \phi)^2}{1 + \frac{s R_a B}{R_a B + (K_a \phi)^2} T_m} = \frac{k_m}{1 + s T_{m1}}, \quad \boxed{\frac{N(s)}{E_a(s)} = \frac{k_m}{1 + s T_{m1}}}$$

$$T_{m1} = \frac{R_a B T_m}{R_a B + (K_a \phi)^2}, \quad k_m = \frac{K_a \phi}{(K_a \phi)^2 + R_a B}$$


$T_{m1} \ll T_m$, neglecting T_L

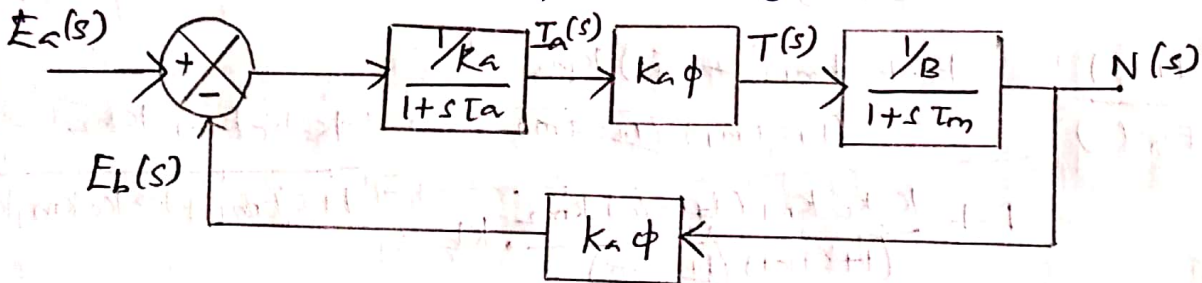

$$\frac{N(s)}{I_a(s)} = \frac{1/B}{1+sT_m} \times K_a \phi = \frac{K_a \phi / B}{1+sT_m} = \frac{k_{m2}}{1+sT_m}, \quad k_{m2} = \frac{K_a \phi}{B}$$

$$\frac{I_a(s)}{E_a(s)} = \frac{N(s)}{E_a(s)} \times \frac{I_a(s)}{N(s)} = \frac{k_m}{1+sT_{m1}} \times \frac{(1+sT_m)B}{K_a \phi} = \frac{k_{m1} (1+sT_m)}{1+sT_{m1}}$$

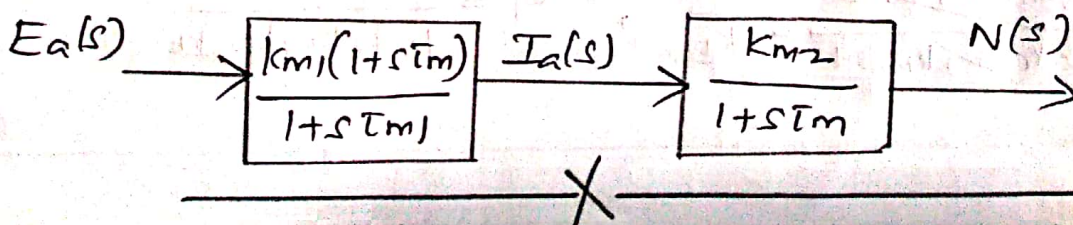
$$\boxed{\frac{I_a(s)}{E_a(s)} = \frac{k_{m1} (1+sT_m)}{1+sT_{m1}}}, \quad k_{m1} = \frac{k_{m2} B}{K_a \phi}, \quad k_m = k_{m1} \times k_{m2}$$



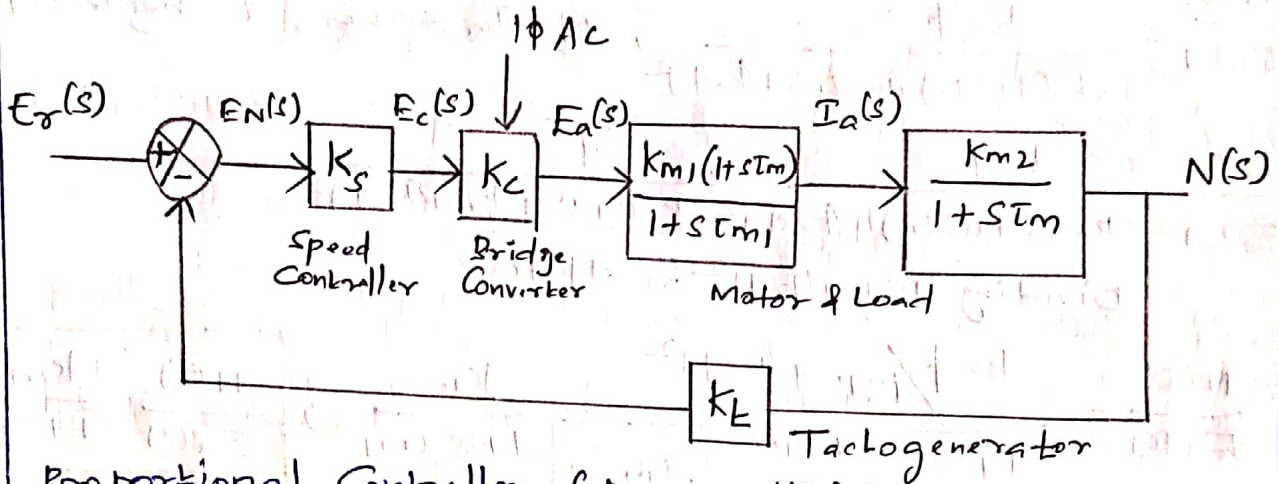2. Design of Speed Controller:



If a dc tachogenerator is attached to Motor shaft, a speed signal fed back to back emf and Error $E_r(s)$ control the Armature voltage via speed controller and 1ϕ & 2ϕ Converter (i) chopper.



Proportional Controller (P-controller)
 proportional Integral Controller (PI)

P- Controller:

$$G_1(s) = K_s K_c \frac{K_{m1}(1+sT_{m1}) K_{m2}}{1+sT_{m1} \times 1+sT_{m2}}$$

$$H(s) = K_t$$

$$\frac{N(s)}{E_r(s)} = \frac{G_1(s)}{1 + G_1(s) H(s)}$$

$$\frac{N(s)}{E_r(s)} = \frac{K_s K_c K_{m1} (1+sT_{m1}) K_{m2}}{(1+sT_{m1})(1+sT_{m2})}$$

$$1 + \frac{K_s K_c K_{m1} (1+sT_{m1}) K_{m2}}{(1+sT_{m1})(1+sT_{m2})} \cdot K_t = \frac{K_s K_c K_{m1} K_{m2}}{1+sT_{m1} + K_s K_c K_{m1} K_{m2} K_t}$$

Dividing by $1 + K_s K_c K_{m1} K_{m2} K_t$

$$\frac{N(s)}{E_r(s)} = \frac{K_s K_c K_{m1} K_{m2}}{1 + s \frac{T_{m1}}{1 + K_s K_c K_{m1} K_{m2} K_t}} = \frac{K_1}{1 + s T_1}$$

$$K_1 = \frac{K_s K_c K_{m1} K_{m2}}{1 + K_s K_c K_{m1} K_{m2} K_t}, \quad K_s K_c K_{m1} K_{m2} K_t \gg 1, \text{ neglect } 1$$

$$K_1 = \frac{K_s K_c K_{m1} K_{m2}}{K_s K_c K_{m1} K_{m2} K_t} = \frac{1}{K_t}, \quad T_1 = \frac{T_{m1}}{K_s K_c K_{m1} K_{m2} K_t}$$

$$\frac{I_a(s)}{N(s)} = \frac{1 + s\tau_m}{k_{m2}}$$

$$\frac{I_a(s)}{E_r(s)} = \frac{N(s)}{E_r(s)} \times \frac{I_a(s)}{N(s)} = \frac{k_1}{1 + s\tau_1} \times \frac{1 + s\tau_m}{k_{m2}} = \frac{k_1(1 + s\tau_m)}{k_{m2}(1 + s\tau_1)}$$

$$\therefore I_a(s) = \frac{k_1(1 + s\tau_m)}{k_{m2}(1 + s\tau_1)} \cdot E_r(s), \quad E_r(s) \text{ Ideal Input} = \frac{E_r}{s}$$

$$I_a(s) = \frac{k_1(1 + s\tau_m)}{k_{m2}(1 + s\tau_1)} \cdot \frac{E_r}{s} = \frac{k_1 E_r (1 + s\tau_m)}{k_{m2} s (1 + s\tau_1)} = \frac{k_1 E_r (1 + s\tau_m)}{k_{m2} s \tau_1 \left(\frac{1}{\tau_1} + s\right)}$$

$\div k_{m2} \tau_1$ both numerator & denominator

Using partial fraction

$$\frac{I_a(s)}{k_{m2} \tau_1} = \frac{\frac{k_1 E_r}{k_{m2} \tau_1} (1 + s\tau_m)}{\frac{k_{m2} s \tau_1}{k_{m2} \tau_1} \left(s + \frac{1}{\tau_1}\right)} = \frac{A_1}{s} + \frac{A_2}{s + \frac{1}{\tau_1}} = \frac{A_1 \left(s + \frac{1}{\tau_1}\right) + A_2}{s \left(s + \frac{1}{\tau_1}\right)}$$

$$\frac{k_1 E_r (1 + s\tau_m)}{k_{m2} \tau_1} = A_1 \left(s + \frac{1}{\tau_1}\right) + A_2 s$$

$$\frac{k_1 E_r}{k_{m2} \tau_1} + \frac{s k_1 E_r \tau_m}{k_{m2} \tau_1} = A_1 s + \frac{A_1}{\tau_1} + A_2 s = (A_1 + A_2) s + \frac{A_1}{\tau_1}$$

Equate Constant term $\rightarrow \frac{k_1 E_r}{k_{m2} \tau_1} = \frac{A_1}{\tau_1}, \therefore A_1 = \frac{k_1 E_r \tau_1}{k_{m2} \tau_1} = \frac{k_1 E_r}{k_{m2}}$

Equate 's' term $\rightarrow \frac{k_1 E_r \tau_m}{k_{m2} \tau_1} = A_1 + A_2 = \frac{k_1 E_r}{k_{m2}} + A_2$

$$A_2 = \frac{k_1 E_r}{k_{m2}} \left(\frac{\tau_m}{\tau_1} - 1\right)$$

$$I_a(s) = \frac{k_1 E_r}{k_{m2} s} + \left[\frac{k_1 E_r}{k_{m2}} \left(\frac{\tau_m}{\tau_1} - 1\right) \right] \frac{1}{\left(s + \frac{1}{\tau_1}\right)}$$

$$= \frac{k_1 E_r}{k_{m2}} \left[\frac{1}{s} + \frac{\tau_m - \tau_1}{\tau_1} \frac{1}{\left(s + \frac{1}{\tau_1}\right)} \right] \rightarrow \text{Taking Inverse Laplace}$$

$$\therefore I_a(k) = \frac{k_1 E_r}{k_{m2}} \left[1 + \frac{\tau_m - \tau_1}{\tau_1} \cdot e^{-k/\tau_1} \right]$$

$$\therefore I_a(\infty) = \frac{k_1 E_r}{k_{m2}} \left[1 + \frac{\tau_m - \tau_1}{\tau_1} e^{-\infty} \right] = \frac{k_1 E_r}{k_{m2}}$$

$$\frac{I_a(k)}{I_a(\infty)} = \frac{\frac{k_1 E_r}{k_{m2}} \left[1 + \frac{\tau_m - \tau_1}{\tau_1} \cdot e^{-k/\tau_1} \right]}{\frac{k_1 E_r}{k_{m2}}} = \boxed{1 + \left(\frac{\tau_m - \tau_1}{\tau_1}\right) e^{-k/\tau_1}} \quad (3)$$

3. Armature Voltage Control & Field Weakening Mode With closed loop Speed Control of Dc Drive

DACE
Cultivating Technology

In closed loop block diagram of speed control
 (i) Below the Base speed (ii) Above the Base speed.

Loop consist of Inner current loop.
 ↳ outer speed loop.

Below the Base speed → Constant Field Current
 Variable Armature voltage

Above the Base speed → Constant Armature voltage
 Variable Field Current

Fully Controlled Converter Forward Braking is not
 PI Controller is mostly used good steady state accuracy & ^{possible} filter out noise

Below the Base speed:

E_{ref} (0.95 to 0.95) of Rated Armature voltage
 (E_{ref}) compared with (E_b) → E_{err} → At rated operation
 → α is zero, reference speed → current limiter saturates & set
 maximum value of permissible current.

If drive accelerating to set point → speed ↑ with E_{ref}
 current limiter desaturates → $T_m = T_L$


If speed ↓ ref, $I_{ref} \rightarrow 0$, drive decelerate to load torque.

Above the Base speed:

When speed of the motor is closer to
 base speed, the field controller comes out of saturation
 reference speed set point chosen to be higher than base speed.
 current limiter sets the corresponding maximum
 permissible value of reference current, $\alpha \downarrow$, $V_a \uparrow$ the
 motor starts accelerating & $\uparrow E_b$.

When (V_a) small when small → high value of field time constant

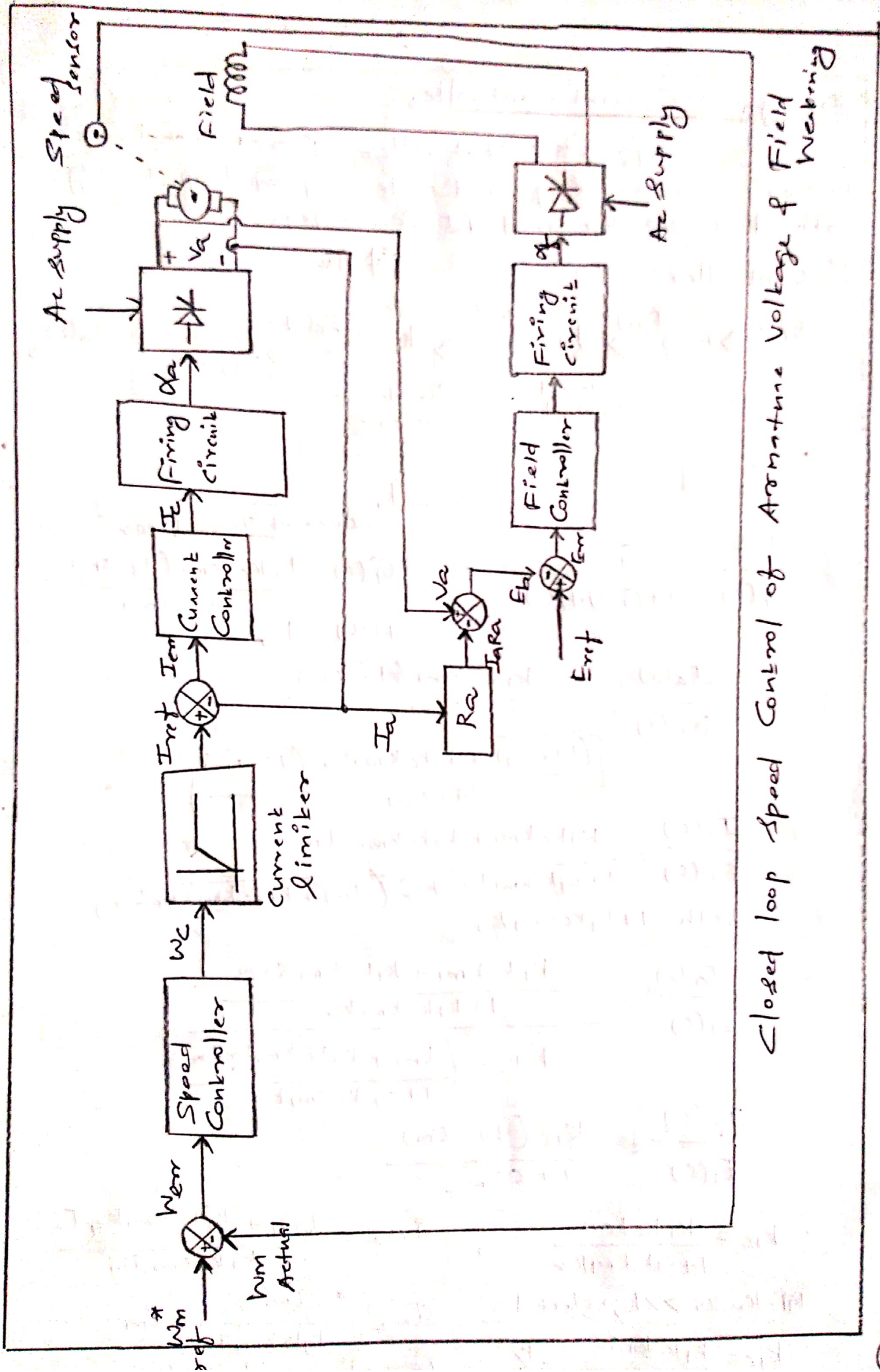Maintaining V_a constant & varying field, speed of the
 motor above base speed.




Closed loop Speed Control of Armature Voltage & Field Weakening

4. Design of Current Controller:

In this controller first construct inner current loop and outer speed loop. Using both P Controller and PI Controller.

P-Controller:

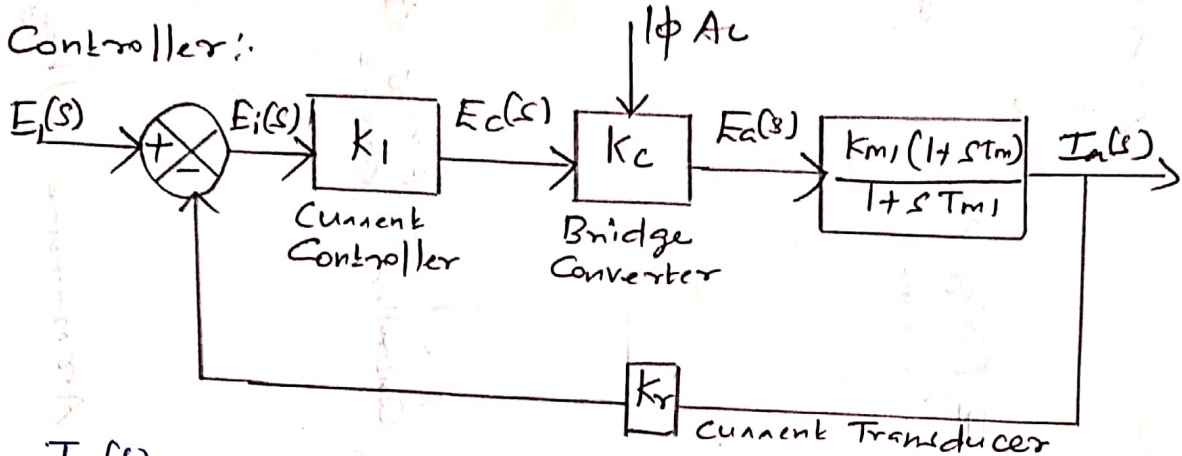

$$\frac{I_a(s)}{E_r(s)} = \frac{G(s)}{1 + G(s) \cdot H(s)}, \quad G(s) = \frac{k_1 k_c k_{m1} (1 + sT_{m1})}{1 + sT_{m1}}$$

$$H(s) = k_r$$

$$\frac{I_a(s)}{E_r(s)} = \frac{k_1 k_c k_{m1} (1 + sT_{m1})}{1 + sT_{m1} + [k_1 k_c k_{m1} k_r (1 + sT_{m1})]}$$

$$\frac{I_a(s)}{E_r(s)} = \frac{k_1 k_c k_{m1} + k_1 k_c k_{m1} sT_{m1}}{1 + k_1 k_c k_{m1} k_r + s(T_{m1} + k_1 k_c k_{m1} k_r T_{m1})}$$

both $1 + k_1 k_c k_{m1} k_r$

$$\frac{I_a(s)}{E_i(s)} = \frac{k_1 k_c k_{m1} + k_1 k_c k_{m1} sT_{m1}}{1 + s \left(\frac{T_{m1} + k_1 k_c k_{m1} k_r T_{m1}}{1 + k_1 k_c k_{m1} k_r} \right)}$$

$$\frac{I_a(s)}{E_i(s)} = \frac{K_{ic} (1 + sT_{m2})}{1 + sT_{m2}}$$

$$\therefore K_{ic} = \frac{k_1 k_c k_{m1}}{1 + k_1 k_c k_{m1} k_r}$$

$k_1 k_c k_{m1} k_r \gg 1$, neglect 1

$$K_{ic} = \frac{k_1 k_c k_{m1}}{k_1 k_c k_{m1} k_r} = \frac{1}{k_r}$$



$$T_{m2} = \frac{T_{m1} + k_1 k_c k_{m1} k_r T_{m1}}{k_1 k_c k_{m1} k_r}$$

$$T_{m2} = \frac{T_{m1}}{k_1 k_c k_{m1} k_r} + T_{m1}$$

$T_{m2} \gg T_{m1}$, neglect T_{m1}

$$\frac{I_a(s)}{E_1(s)} = \frac{k_{ic}(1+sT_m)}{1+sT_m} = \frac{1+sT_m}{k_r(1+sT_m)} = \frac{1}{k_r} = k_{ic} \therefore k_{ic} = \frac{1}{k_r}$$

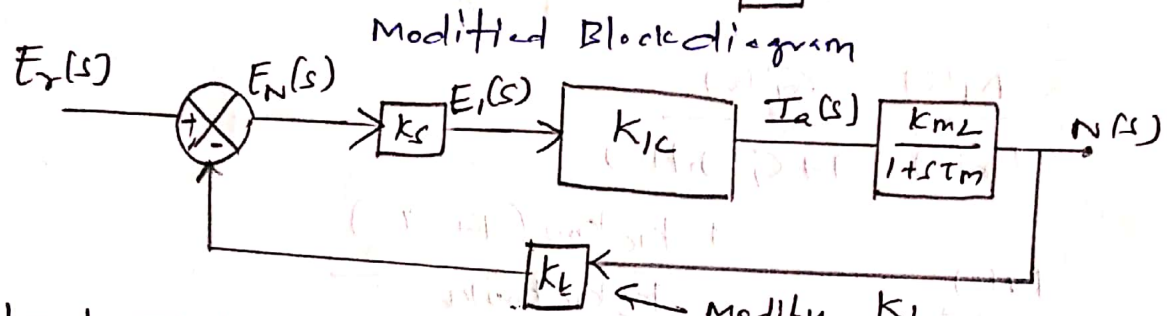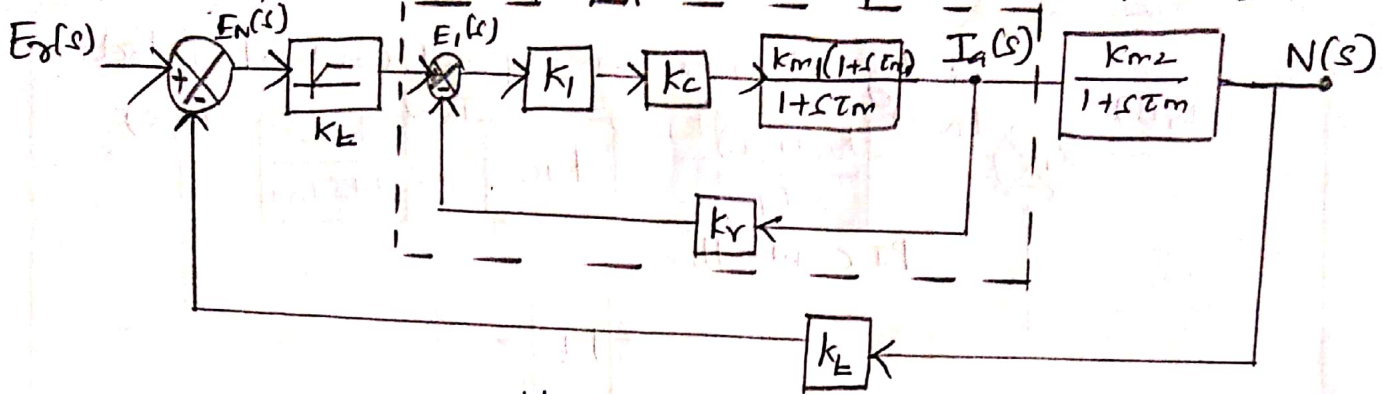Now Add with inner loop & outer loop (Current & speed)



Without Tachogenerator:

$$\frac{N(s)}{E_r(s)} = \frac{k_2}{1+sT_2} \quad \therefore k_2 = \frac{k_c k_{ic} k_{m2}}{k_s k_e k_r k_{m1} k_E}, \quad k_2 = \frac{1}{k_E}$$

$k_s k_e k_r k_{m1} k_E \gg 1$, neglect 1

$$\frac{I_a(s)}{E_r(s)} = \frac{N(s)}{E_r(s)} \times \frac{I_a(s)}{N(s)} \quad T_2 = \frac{T_m}{k_s k_{ic} k_{m2} k_E}$$

$$= \frac{k_2}{1+sT_2} \times \frac{1+sT_m}{k_{m2}} = \frac{k_2(1+sT_m)}{k_{m2}(1+sT_2)}$$

$$\frac{N(s)}{I_a(s)} = \frac{k_{m2}}{1+sT_m}, \quad N(s) = \frac{k_{m2}}{1+sT_m} \cdot \frac{I_a(s)}{s}$$


Tachogenerator with Filter:

$$\frac{N(s)}{E_r(s)} = \frac{k_s k_E k_{m2} k_{ic} (1+sT_E)}{\left(1 + \frac{s(T_E + T_m)}{k_i} + \frac{s^2 T_m T_E}{k_i}\right) (1 + k_E k_s k_{m2} k_{ic})}$$

$$\frac{I_a(s)}{E_r(s)} = \frac{N(s)}{E_r(s)} \times \frac{I_a(s)}{N(s)}, \quad \frac{1+sT_m}{k_{m2}} = \frac{I_a(s)}{N(s)}$$

$$\frac{I_a(s)}{E_r(s)} = \frac{k_s k_{ic} (1+sT_E) (1+sT_m)}{(1 + k_E k_s k_{m2} k_{ic}) \left[1 + \frac{s(T_E + T_m)}{k_i} + \frac{s^2 T_m T_E}{k_i}\right]}$$

PI Controller:

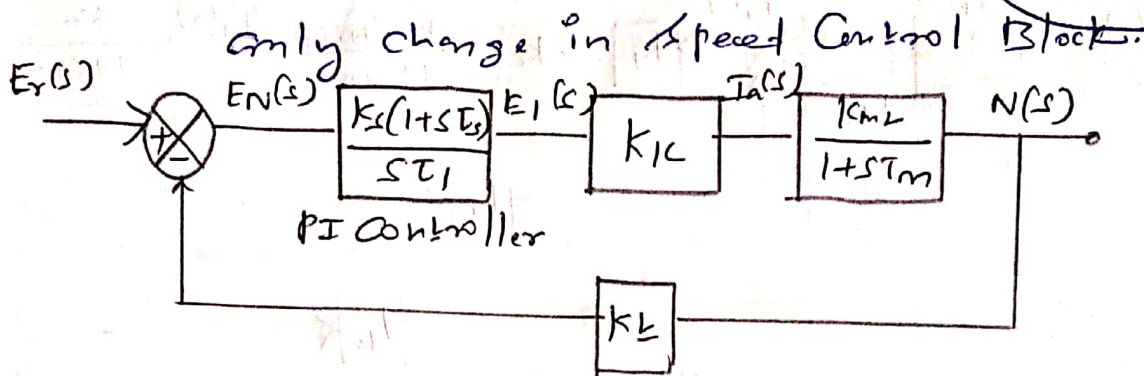

$$\frac{N(s)}{E_r(s)} = \frac{G(s)}{1 + G(s) \cdot H(s)}$$

$$\frac{N(s)}{E_r(s)} = \frac{k_s k_{ic} k_{m2} (1 + sT_s)}{k_s k_{ic} k_{m2} k_e} \cdot \frac{1}{1 + sT_s (1 + k_s k_{ic} k_{m2} k_e)} + \frac{s^2 T_s T_m}{k_s k_{ic} k_{m2} k_e}$$

$$\frac{N(s)}{E_r(s)} = \frac{1}{k_e} \frac{(1 + sT_s)}{1 + sT_s + s^2 T_s T_2} = \frac{1}{k_e} \frac{1 + sT_s}{1 + sT_s + s^2 T_s T_2}$$


$$\frac{I_a(s)}{E_r(s)} = \frac{N(s)}{E_r(s)} \times \frac{I_a(s)}{N(s)}, \quad \frac{I_a(s)}{N(s)} = \frac{1 + sT_m}{k_{m2}}$$

$$\frac{I_a(s)}{E_r(s)} = \frac{1}{k_e} \frac{1 + sT_s}{1 + sT_s + s^2 T_s T_2} \times \frac{1 + sT_m}{k_{m2}}$$

$$\frac{I_a(s)}{E_r(s)} = \left(\frac{1}{k_e k_{m2}} \right) \frac{(1 + sT_s)(1 + sT_m)}{(1 + sT_s + s^2 T_s T_2)}$$

————— X —————

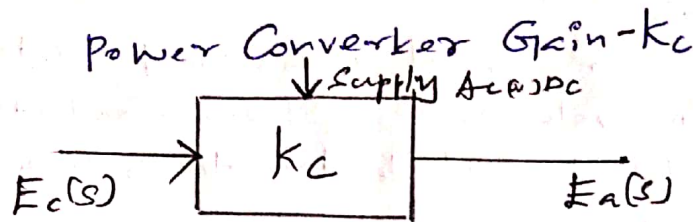5. Transfer Function of power Converter:-



Converter Transfer function $G_c(s) = \frac{E_a(s)}{E_c(s)}$

K_c - Converter gain

T_c - Converter time delay

s - Laplace operator

$$G_c(s) = \frac{K_c}{1 + sT_c}$$

Converter gain for maximum Control voltage E_{cm}

(1 ϕ)
$$K_c = \frac{2V_m}{\pi E_{cm}} = \frac{2\sqrt{2}V_s}{\pi E_{cm}}$$

$$K_c = 0.9 \frac{V_s}{E_{cm}}$$

Where

V_s - 1 ϕ AC voltage

E_{cm} - maximum Control voltage

(3 ϕ)
$$K_c = \frac{3V_m}{\pi E_{cm}} = \frac{3\sqrt{2}V_L}{\pi E_{cm}}$$

$$K_c = \frac{1.35V_L}{E_{cm}}$$

Delay may be treated one half of this Interval

$$T_c = \frac{60/2}{360} \times \text{time period of one cycle}$$

$$T_c = \frac{1}{12} \times \frac{1}{f_s}$$

Converter K_c can be modeled with its gain & time delay

$$G_c(s) = K_c e^{-sT_c}$$

$$G_c(s) = \frac{K_c}{1 + sT_c}$$

6. Converter Selection & characteristics:

Depending upon the specifications of Motor and Load, the ratings of power converter chosen.

I_{max} — motor current is assumed continuous & Rms value of each device conduct 120° electrical. It's not suitable for discontinuous conduction.

RMS Value of current in power device:

$$I_{rms} = \frac{I_{max}}{\sqrt{3}} = 0.5771 I_{max}$$

Voltage rating of device:

$$V_{rg} = \sqrt{2} V \text{ (line to line voltage)}$$

RMS value of fundamental component of supply current I_1 :

$$I_1 = \frac{2\sqrt{3}}{\sqrt{2}\pi} I_{max} = \frac{\sqrt{2}\sqrt{3}}{\pi} I_{max} = 0.78 I_{max}$$

power rating of Converter:

$$P_o = V_o I_{max} = (1.35 V \cos \alpha) I_{max}$$

$$P_o = 1.35 V I_{max} \cos \alpha$$

Assume no loss in Converter: $\therefore \alpha$ - PF angle

$$P_{in} = P_o = \sqrt{3} V I_1 \cos \alpha \quad \text{--- (1)}$$

$$\therefore \text{Reactive power } \phi_i = 1.35 V I_{max} \sin \alpha \quad \text{--- (2)}$$

$$\text{Apparent power } S = \sqrt{(P_i)^2 + (\phi_i)^2}$$

$$S = 1.35 V I_{max} = \sqrt{3} V I_1$$

18